

HSPICE

Memory - SRAM

Yi-Ting Lai


Master Student

**International College of Semiconductor Technology
National Chiao Tung Yang Ming University**

國立陽明交通大學

NATIONAL YANG MING CHIAO TUNG UNIVERSITY

Memory Categories

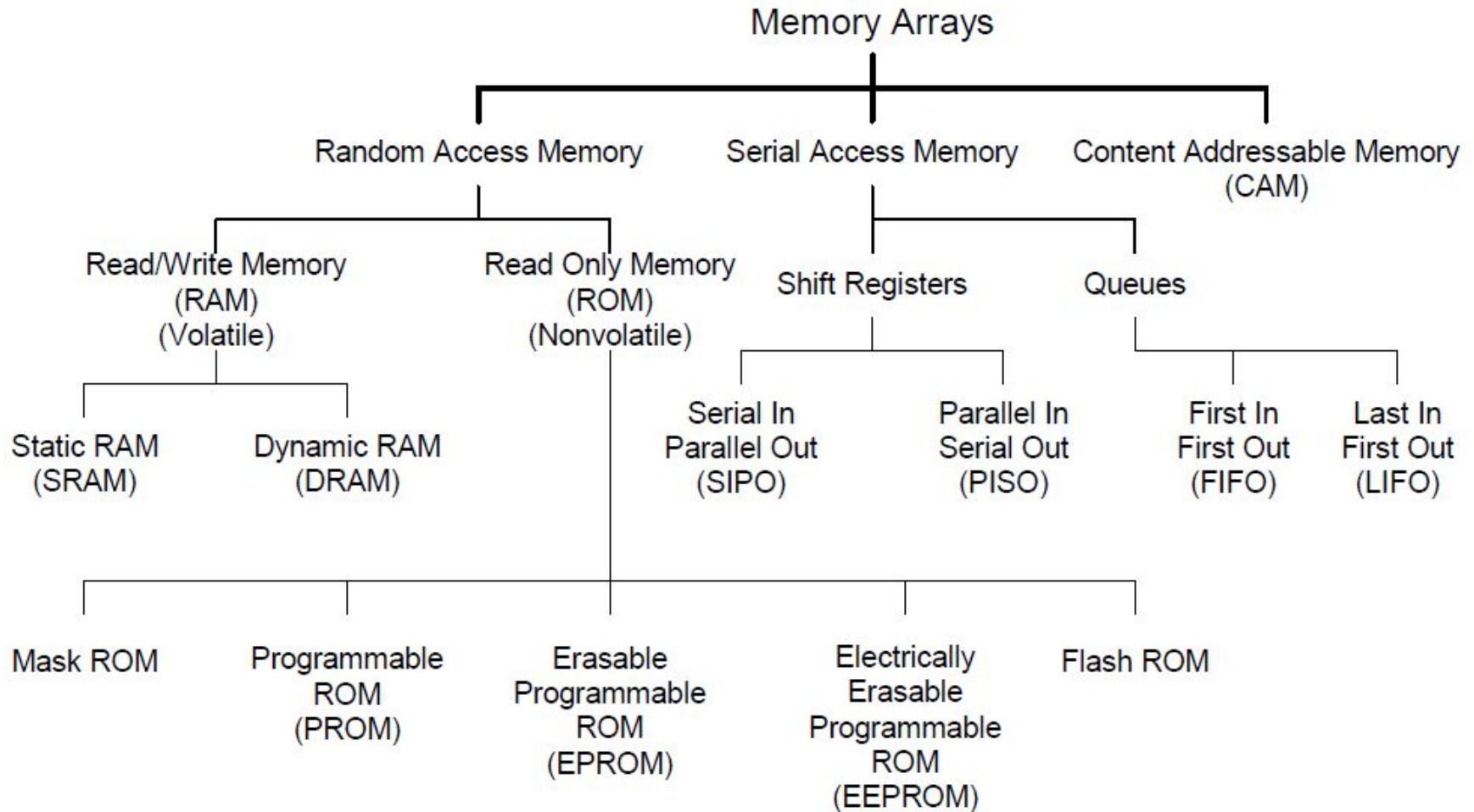

Memory Categories

- RAM: Random Access Memory
 - ◆ Historically defined as memory array with individual bit access
- ROM: Read Only Memory
 - ◆ Write typically requires high voltages or erasing by UV light
- Volatility vs. Non-volatile of Memory
 - ◆ Volatile memory loses data over time or when power is removed (ex: RAM)
 - ◆ Non-volatile memory stores data even when power is removed (ex: ROM)
- Static vs. Dynamic Memory
 - ◆ Static: holds data as long as power is applied (SRAM)
 - ◆ Dynamic: must be refreshed periodically (DRAM)

SRAM Architecture

■ SRAM basic structure


- ◆ SRAM Array

■ SRAM Peripheral Circuits

- ◆ Sense amplifier
- ◆ Write Driver
- ◆ Row decoder
- ◆ Column decoder
- ◆ Timing unit


■ SRAM I/O Latches/FFs

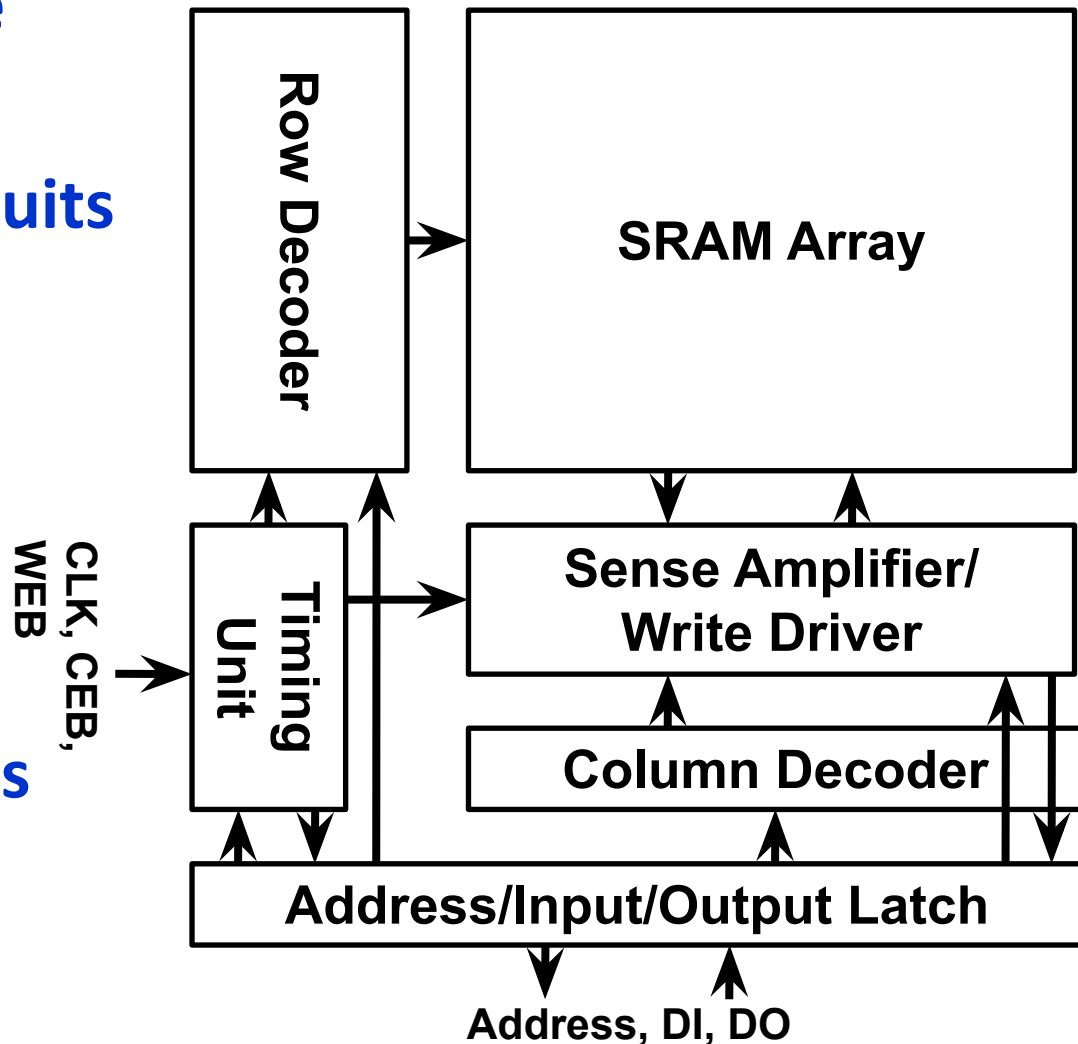- ◆ Address Latch
- ◆ Input latch
- ◆ Output latch



SRAM Array


- 2^n words of 2^m bits each

 

Read Operation in Global Circuits

■ Read Path

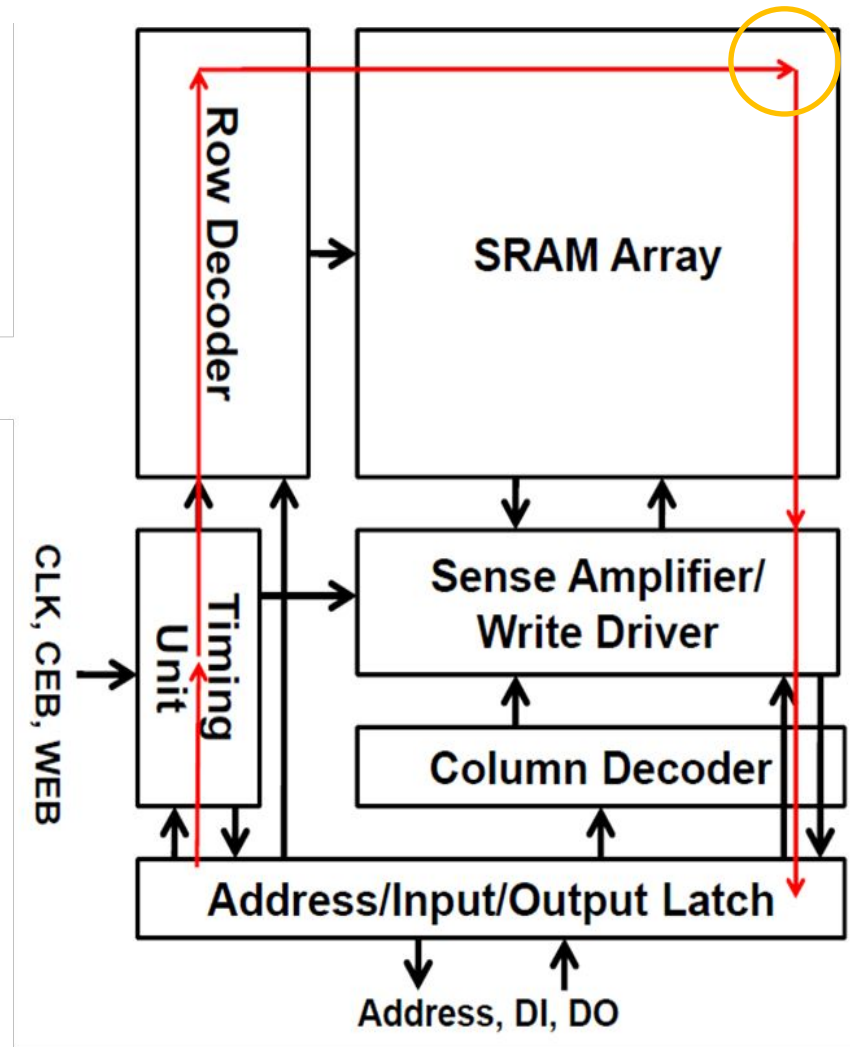- ◆ Address latch
- ◆ Timing Unit
- ◆ Row Decoder (WL driver)
- ◆ SRAM Array
- ◆ Selected WL
- ◆ Selected BL pairs
- ◆ Sense Amplifier
- ◆ Output latch




Write Operation in Global Circuits

■ Data Path

- ◆ Input latch
- ◆ Write Driver
- ◆ SRAM Array (Selected BL pairs)


■ Control Path

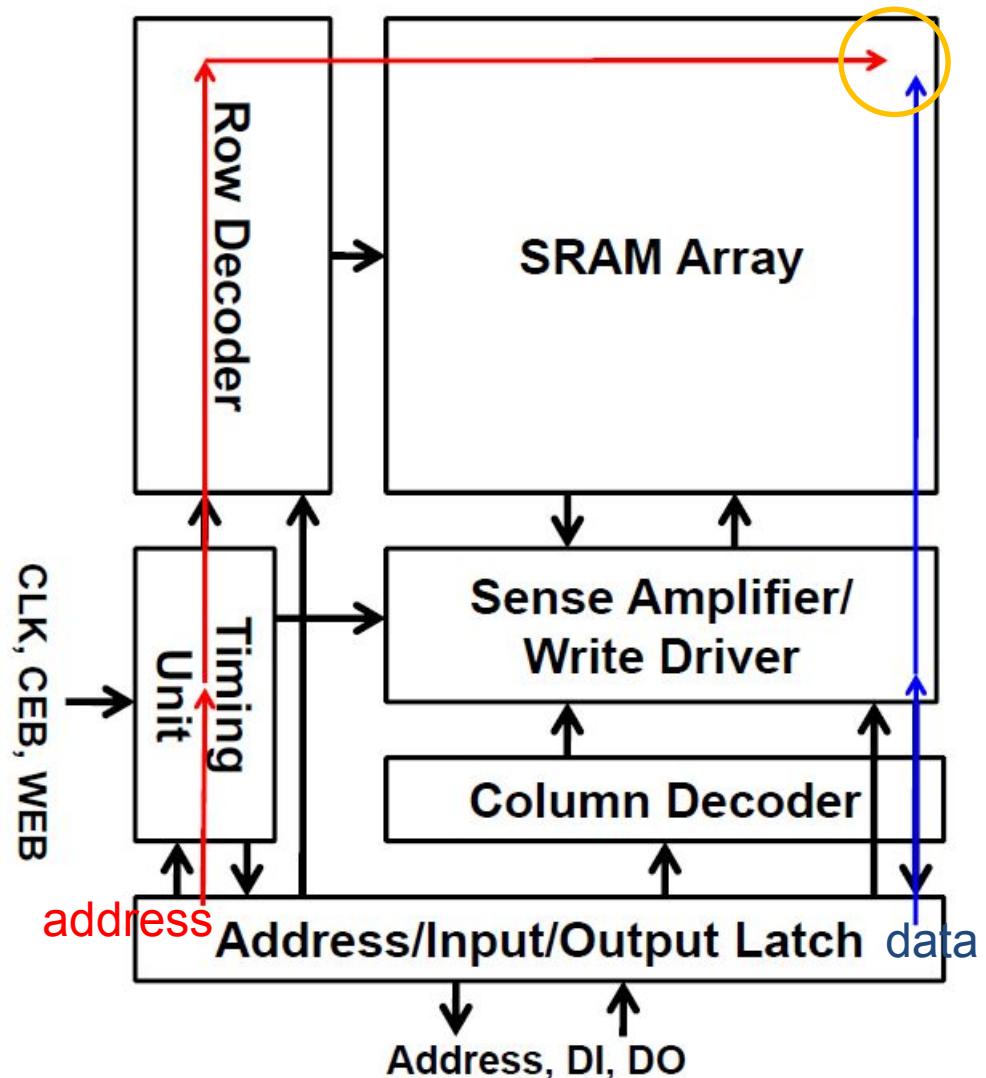- ◆ Address latch
- ◆ Timing Unit
- ◆ SRAM Array (Selected WL)




6T SRAM Cell

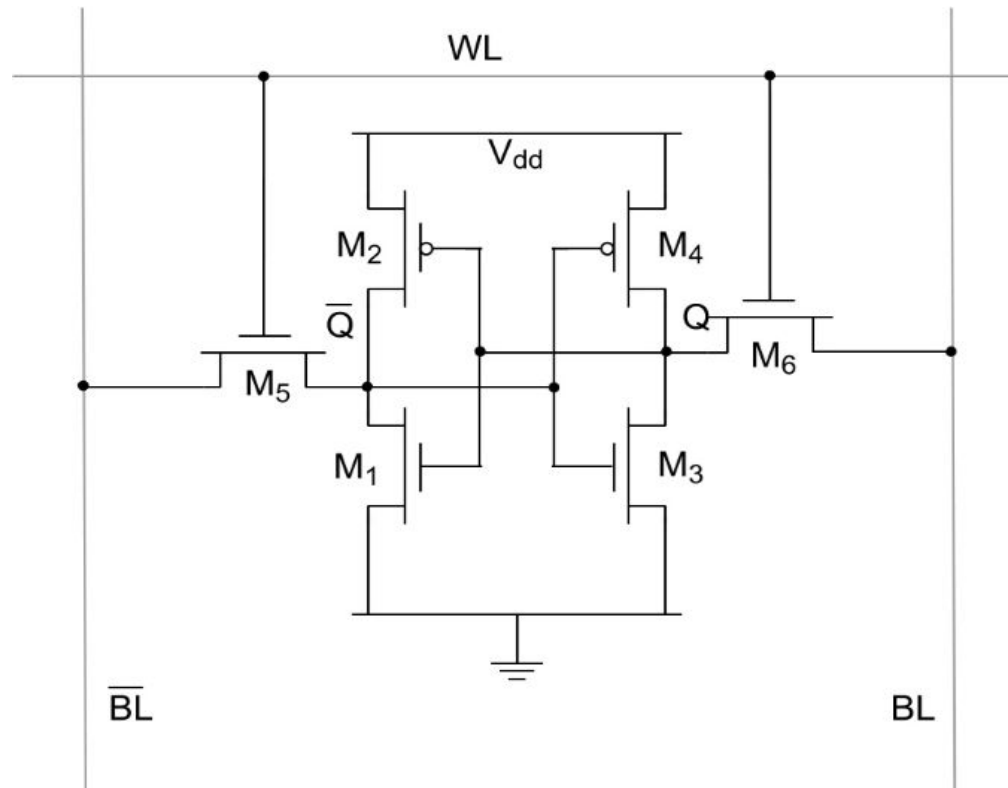- Cross-coupled inverter to latch/store data
- Bi-directional access transistor
 - ◆ ∴ NMOS: "strong 0 weak 1" when passing data
∴ SRAM cell is written through data 0 side.




6T SRAM Cell - Hold

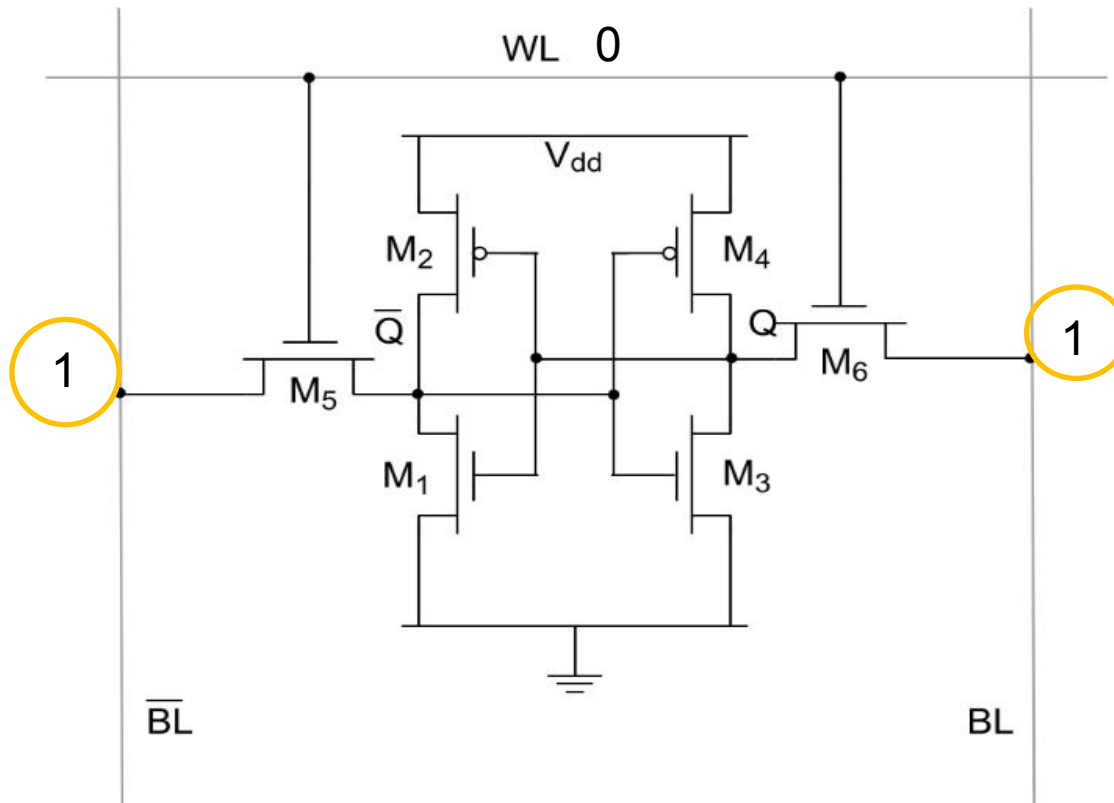- When power on and no read/write operation command input.
- Bit line & bit line bar is pre-charged, preparing for the command input and do the operations.





6T SRAM Cell - Read

- Open word line (pull high) and make the pass transistor opened.
- Data (Q & Q bar) influences bit line & bit line bar. The voltage difference on bit line & bit line bar is small and hard to be sensed by ordinary logic gate correctly. To solve the problem, we need **sense amplifier** at the bottom of array.
- The **sensing time** in read operation is the critical path of the SRAM because there are many cell on the column and each size of MOS in cells is small.

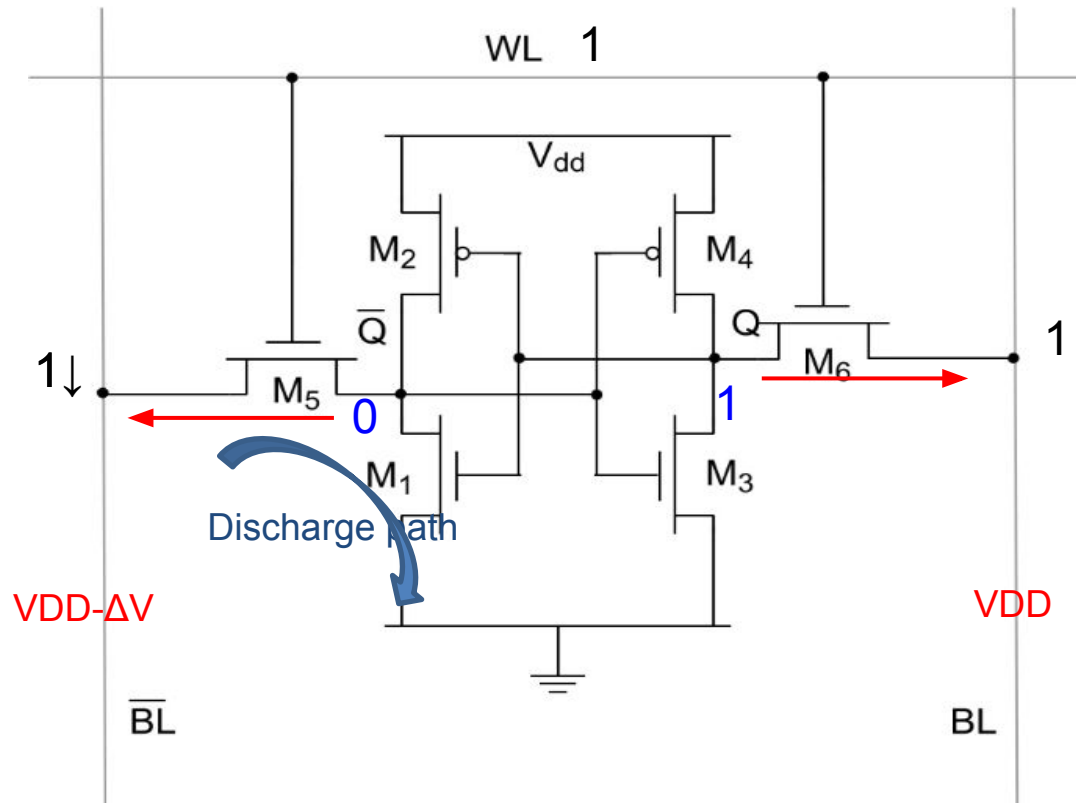

6T SRAM Cell - Write

 
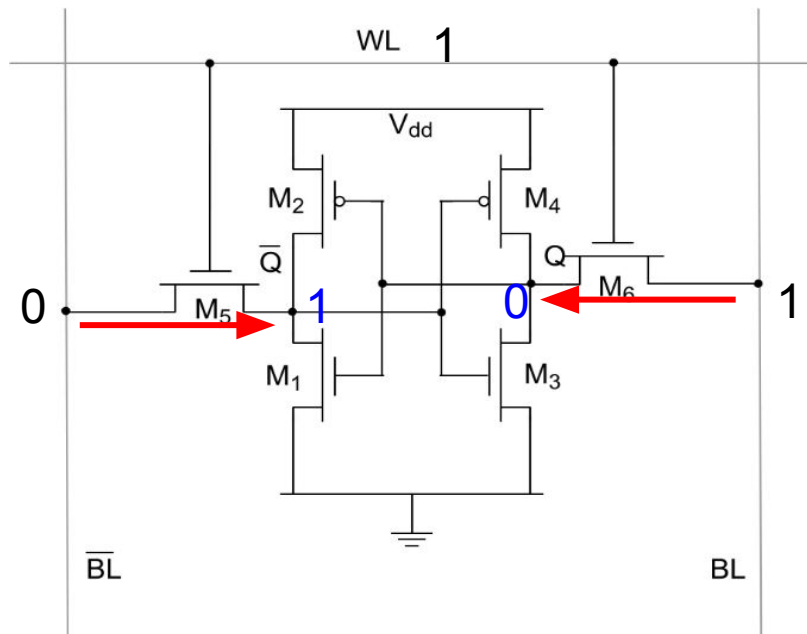
- Write circuit makes bit line & bit line bar transfer to its value.(input 0, input bar 1)
- Open word line and write the value to Q & Q bar.
- Because NMOS pass strong 0 weak 1, the value is written into the cell mainly by “0” side.





Cross the
trigger point

Static Noise Margin (SNM): Butterfly Curve

  
- SNM: The maximum value of “ V_n ” that can be tolerated by the flip-flop before changing state
- Standby (or Retention) SNM: word line low
- Read SNM (RSNM): word line high



  Static Noise Margin (SNM): Butterfly Curve






 SNM is length of side of the largest embedded square on the butterfly curve



E. Seevinck, F. List, J. Lohstroh,
"Static-Noise Margin Analysis of
MOS SRAM Cells" JSSC, Oct '87.

Write-ability and Write Margin

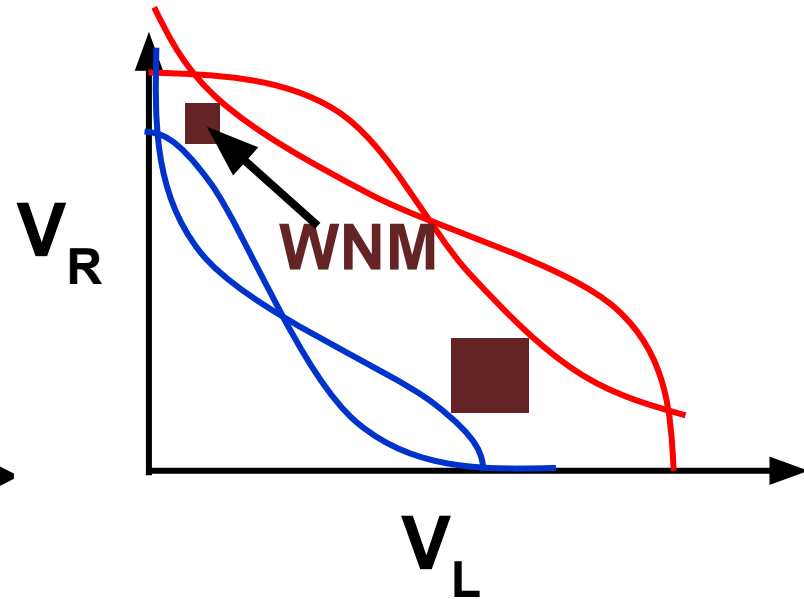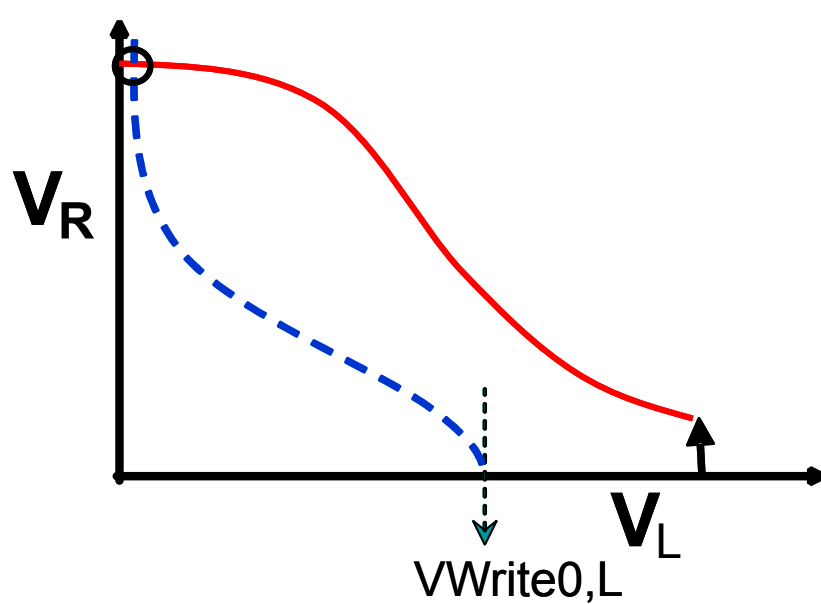 





Exercise

- Using 7nm FinFET model to design an 6T SRAM and measure its WM and HSNM and RSNM
- Show the wave form:


◆ SNM (show signal: v1, v2)

- ④ ☐ Hold SNM
- ⑤ ☐ Read SNM
- ⑥ ☐ Write SNM

WM
HSNM
RSNM

    

Hold

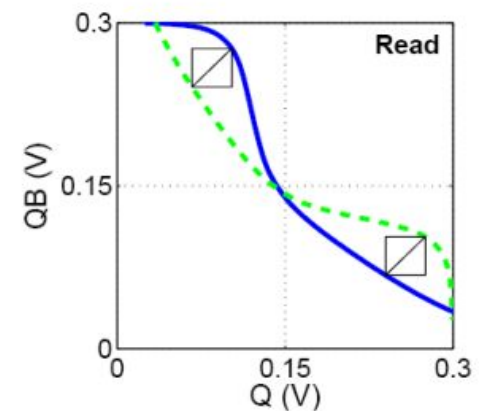

Read

Exercise Notice

② Edit of voltage.

- BL & BLB: I prefer using “.ic” command instead of using ordinary voltage definition because BL & BLB would be floating after pre-charged in the real circuit.


```
.ic V(?? .BL)= ?? * ?? need to be edited  
.ic V(?? .BLB)= ?? * ?? need to be edited
```

- Adding the capacitor on BL & BLB is to make the simulation closer to reality. (if the wave form is weird you can adjust by yourself)


```
CBLB BLB GND BITCAP  
CBL BL GND BITCAP
```


Exercise SNM Wave Form Hint

- Hold SNM wave form :

 

- Read SNM wave form :

 

- Write SNM wave form :

