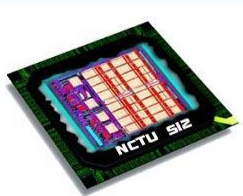


# Introduction to IC Design & Combinational Circuit

---

Lecturer: Zhi-Qi,Huang



# Outline

- ✓ **Section 1 Introduction to design flow**
- ✓ **Section 2 Basic Description of Verilog**
- ✓ **Section 3 Behavior Models of Combinational circuit**
- ✓ **Section 4 Simulations**



# Outline


- ✓ **Section 1 Introduction to design flow**
- ✓ Section 2 Basic Description of Verilog
- ✓ Section 3 Behavior Models of Combinational circuit
- ✓ Section 4 Simulations



# How Does Hardware Accelerate System
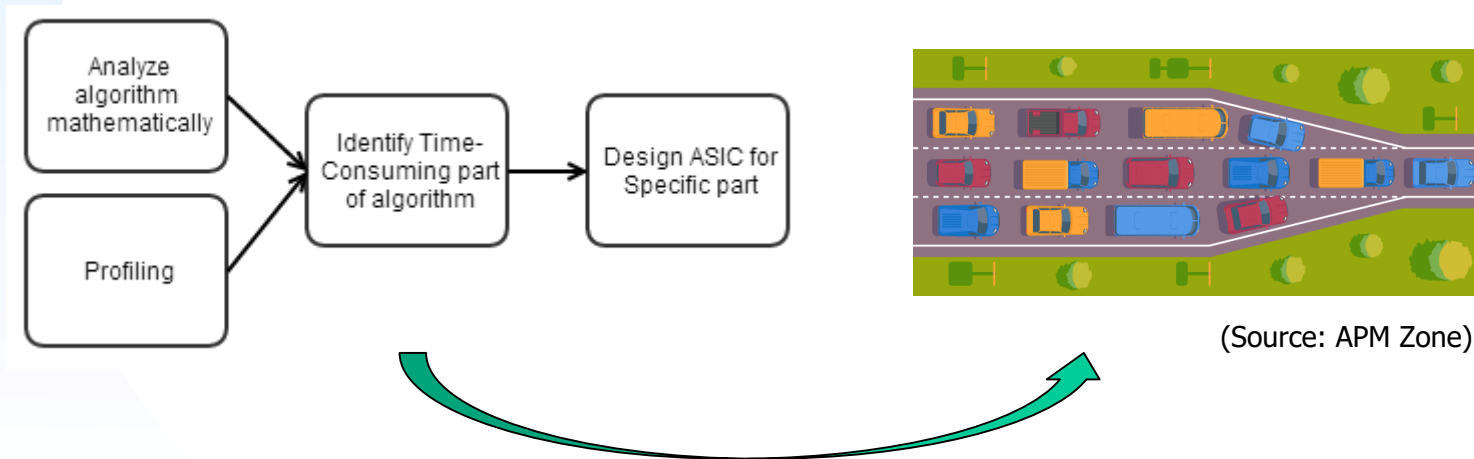
## ✓ Profiling

- Profiling is a form of dynamic program analysis that measures the space/time complexity of a program to aid program optimization.
- By doing profiling we can find the most time-consuming part of the system
- Designers can implement this part in hardware instead of software



# How Does Hardware Accelerate System - Example

✓ An algorithm contains steps:


– (1) → (2) → (3) → (4)

✓ **Mathematical Analysis:**

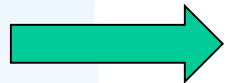- (1) :  $O(C)$
- (2) :  $O(n)$
- (3) :  $O(n^2)$
- (4) :  $O(n)$

✓ **Profiling**

- Running 1000 times takes 100sec
- (1) : 5s
- (2) : 10s
- (3) : 70s
- (4) : 15s




Make ASIC for (3), easily accelerated by 100x

✓ **Profiling with ASIC : Running 1000 times**

- (1) : 5s
- (2) : 10s
- (3) : 0.7s + 0.3s (communication time)
- (4) : 15s



takes 31s

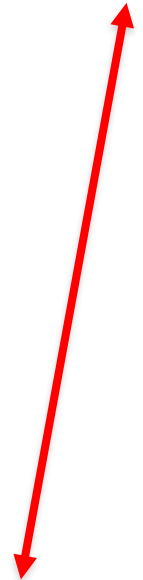


# How Does Hardware Accelerate System

## ✓ Application Specific IC (ASIC)

- Specially designed IC are much faster than general purpose CPU.
- we can design dedicated datapath and controller for the time-consuming part which requires less time
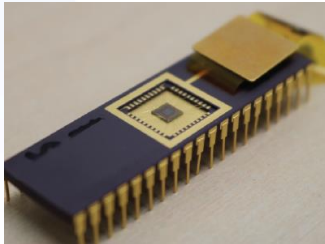
## ✓ Field-Programmable Gate Array(FPGA)

- As implied by the name itself, the FPGA is field programmable.
- FPGA working as a microprocessor can be reprogrammed to function as the graphics card in the field, as opposed to in the semiconductor foundries.



(Source: sigenics)




(Source: Xilinx)

# FPGA Example
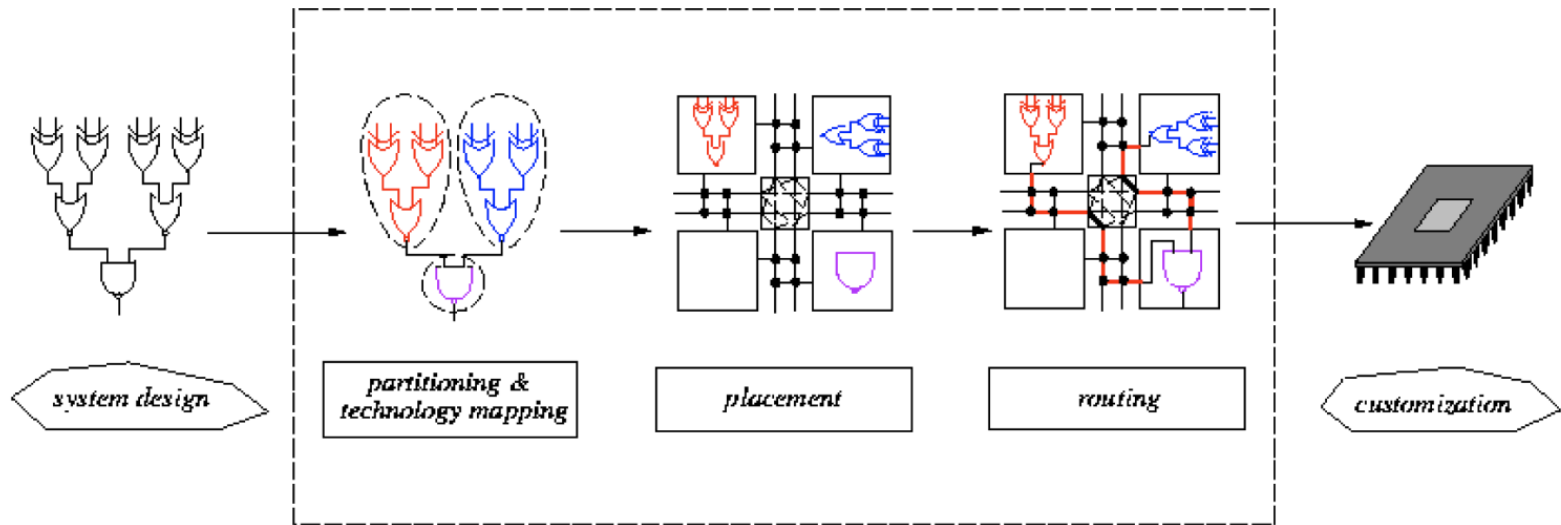
## ✓ FPGA

- No fabrication is needed
- Limited routing resources



*logic + layout synthesis*

(Source: PDA, Prof. Chen)

# ASIC Example

## ✓ Cell-based Design Flow


- use **pre-designed** logic cells (known as standard cells) and micro cells (e.g. microcontroller)
- designers save time, money, and reduce risk



## ✓ Full-Custom Design Flow

- Design everything by yourself
- Not our focus

	Cell-based	Full-Custom
Pro.	Design speed is fast	Large design freedom
Con.	Less design freedom	Design speed is slow

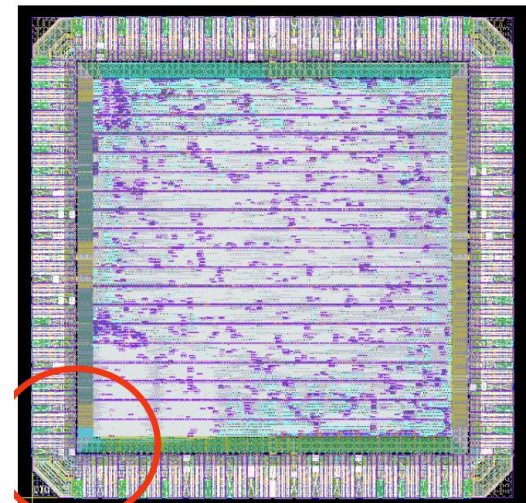

(Source: TSRI)




# Standard Cell Example






# Full-Custom Example


## 4-bit Carry Ripple Adder

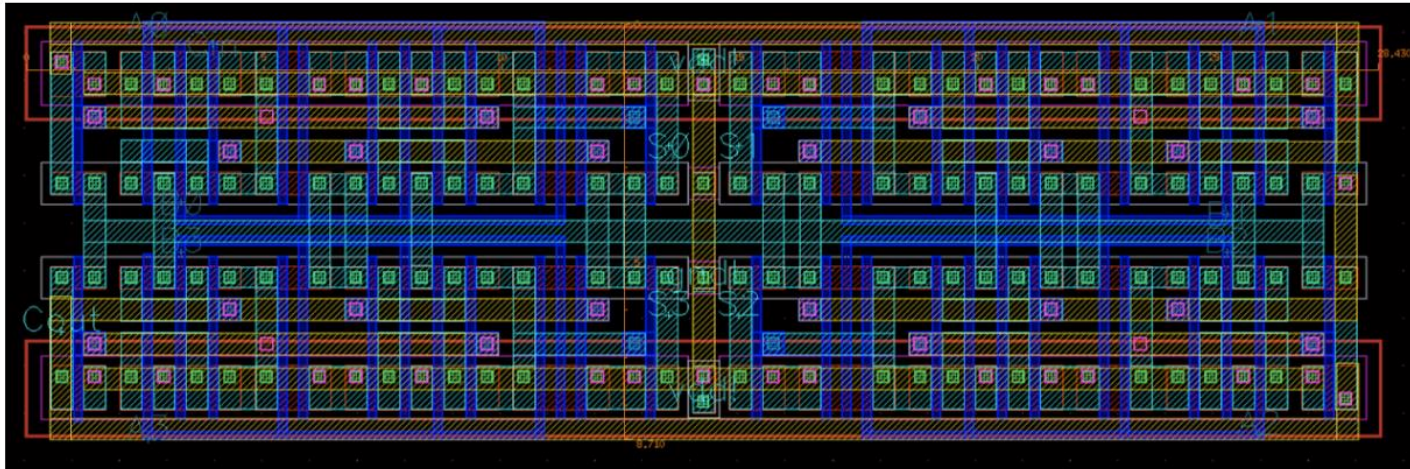

## 4-bit Carry Skip Adder

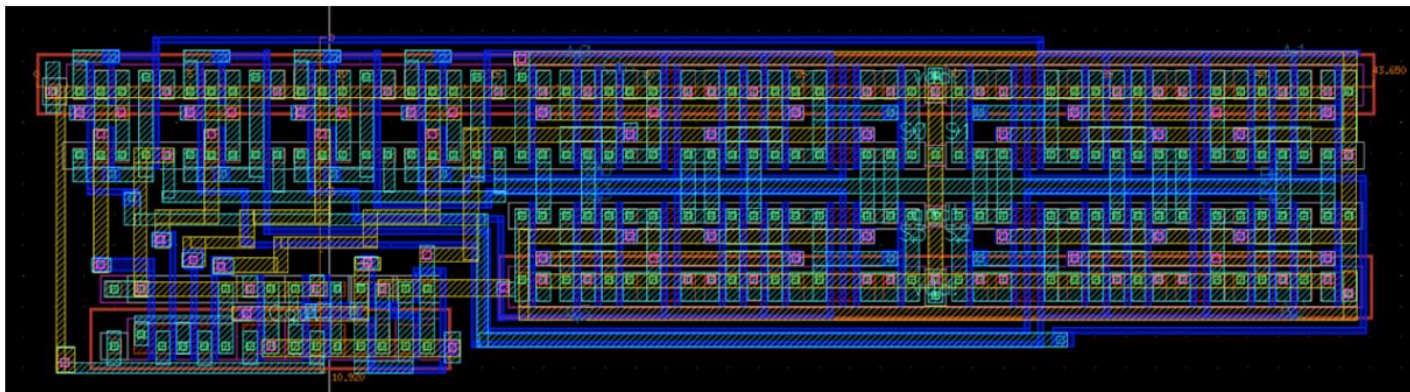

# Cell-based Design Flow

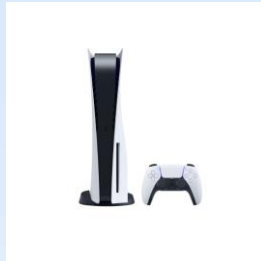

Specification Development  
System models

System Architecture

RTL code development  
Functional Verification

RTL

1

Synthesis  
Timing Verificaiton

Synthesis

2

Physical Synthesis/Place and Route  
Physical Verification

Physical Design


3

Prototype  
Build and Test




System Integration and  
Software Test



# Cell-based Design Flow

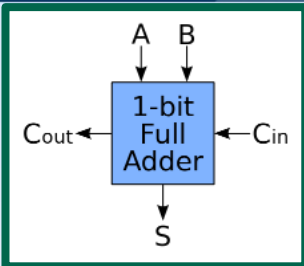
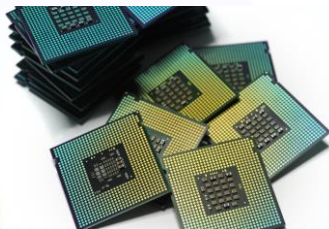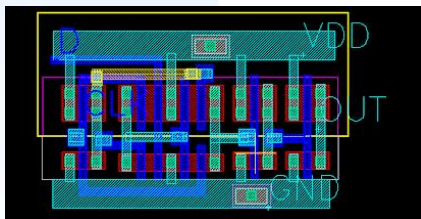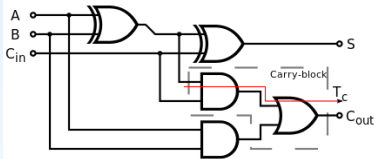
```
module adder(input a,input b,output c);
wire [31:0] a,b;
wire [31:0] c;
assign c = a + b;
endmodule
```



**Specification Development**  
**System models**

System Architecture

**RTL code development**  
**Functional Verification**

RTL

1

**Synthesis**  
**Timing Verificaiton**

Synthesis

2

**Physical Synthesis/Place and Route**  
**Physical Verification**

Physical Design



3

**Prototype**  
**Build and Test**



System Integration and  
Software Test



# Cell-based Design Flow - RTL to GATE

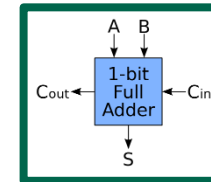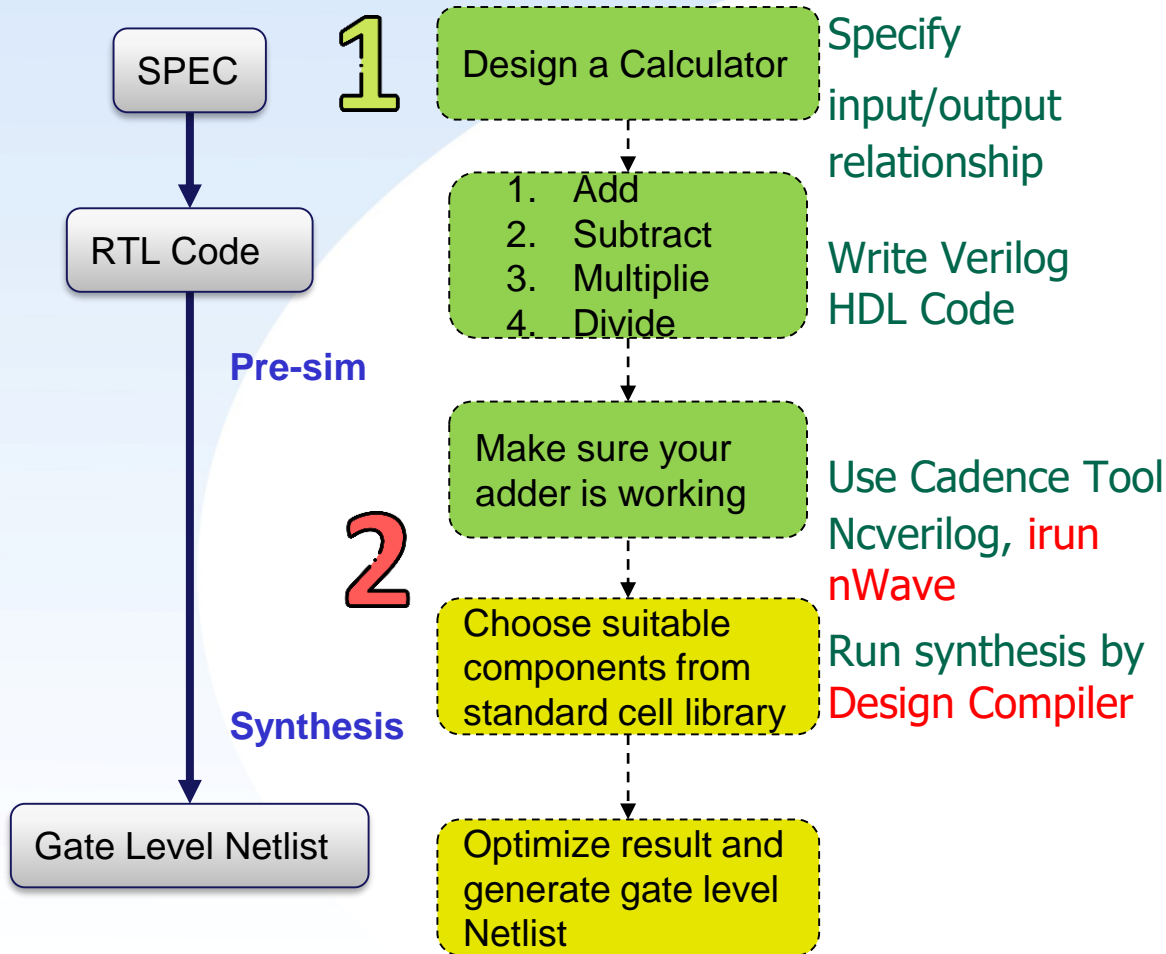

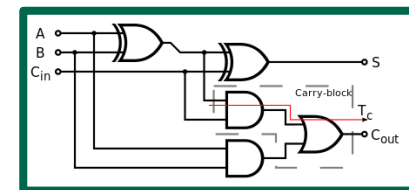
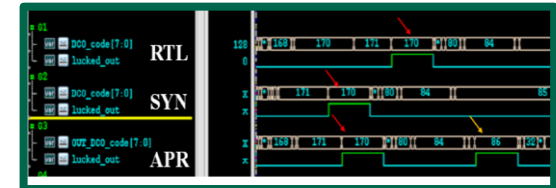
```
module adder(input a,input b,output c);
wire [31:0] a,b;
wire [31:0] c;
assign c = a + b;
endmodule
```





```
NOR2X1 U148 ( .A(n494), .B(n492), .Y(n349) );
AOI22X1 U149 ( .A0(n272), .A1(opt[2]), .B0(n271),
AND2X1 U150 ( .A(n235), .B(n223), .Y(n104) );
INVX2 U151 ( .A(opt[0]), .Y(n295) );
```


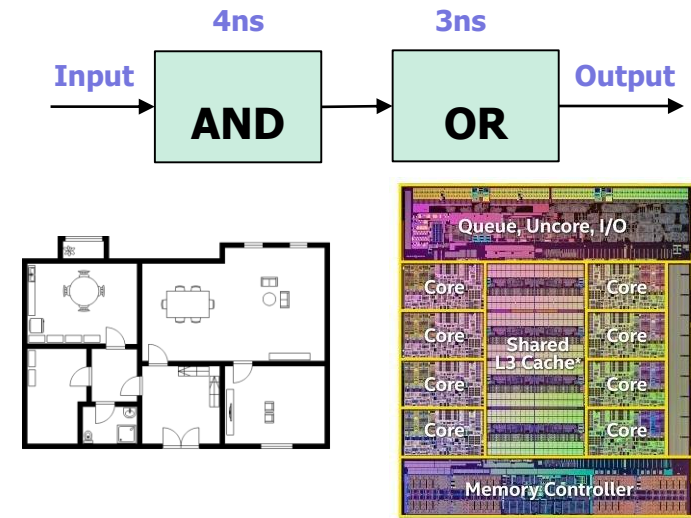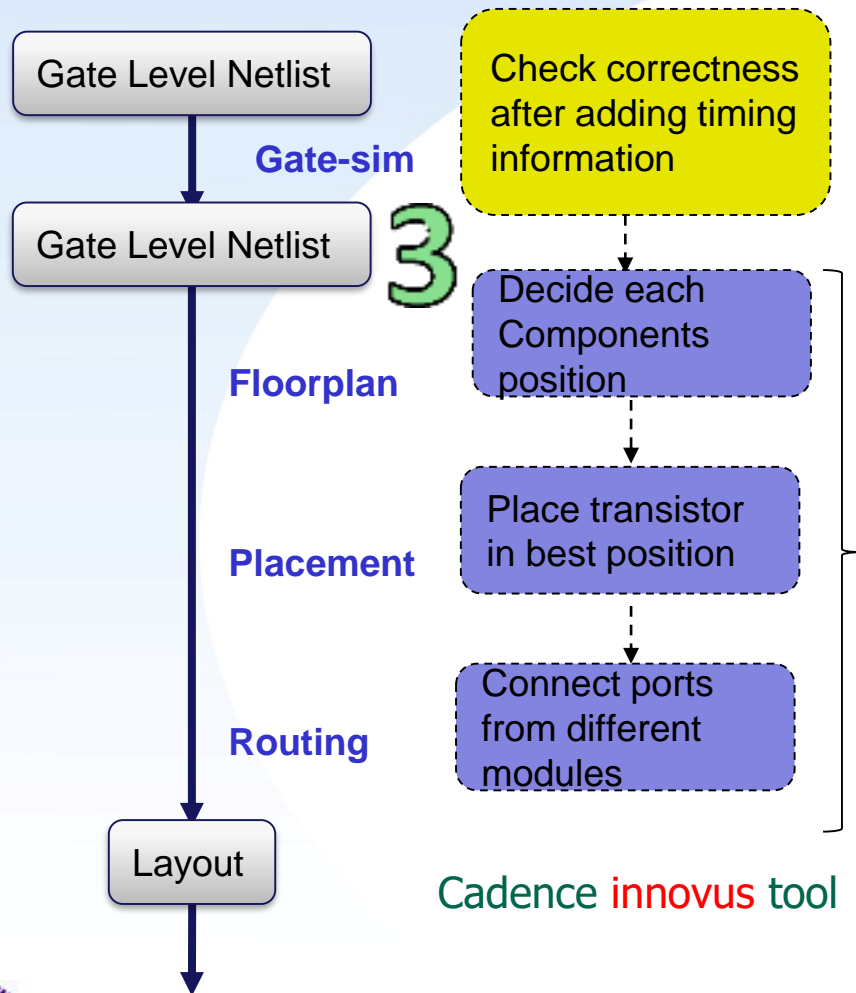
# Cell-based Design Flow – GATE to LAYOUT



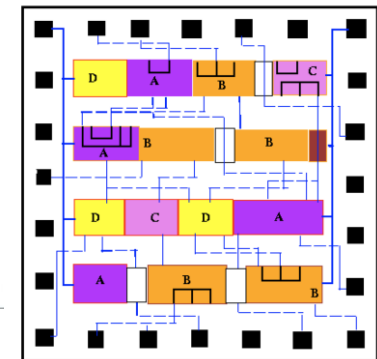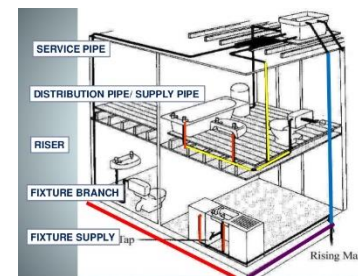
(Source: Intel i7-5960X processor floorplan)





(Source: PDA, Prof. Chen)




# Layout

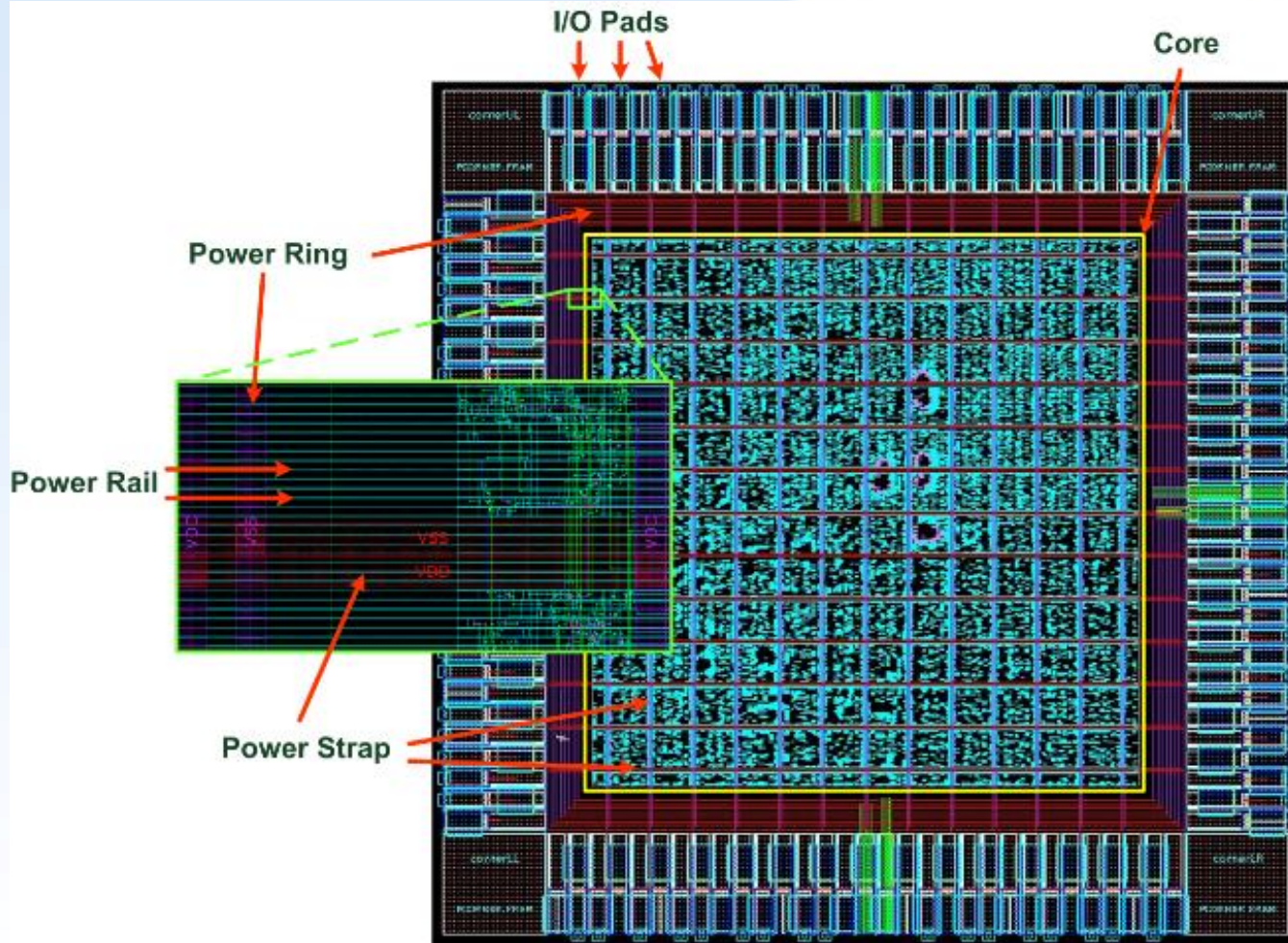
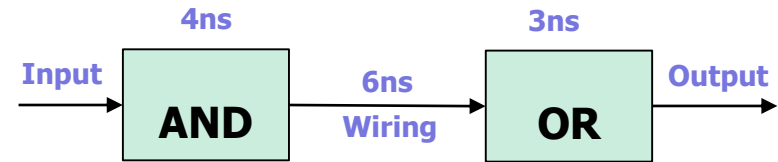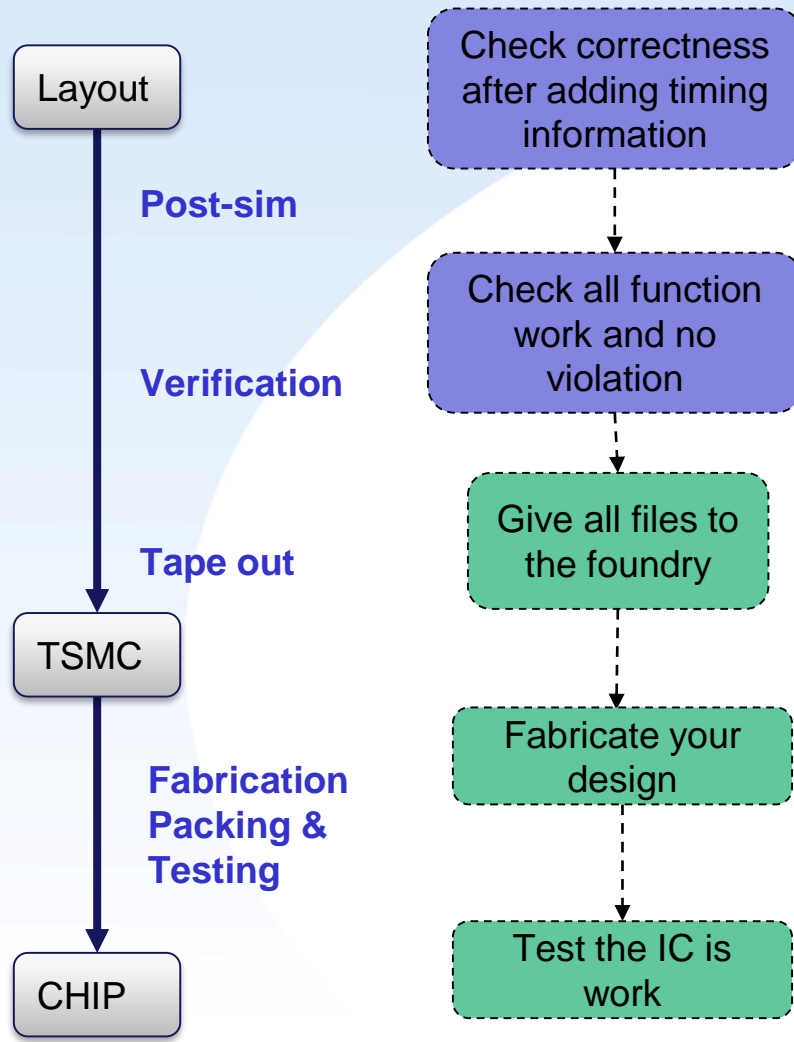
# Cell-based Design Flow – LAYOUT to CHIP



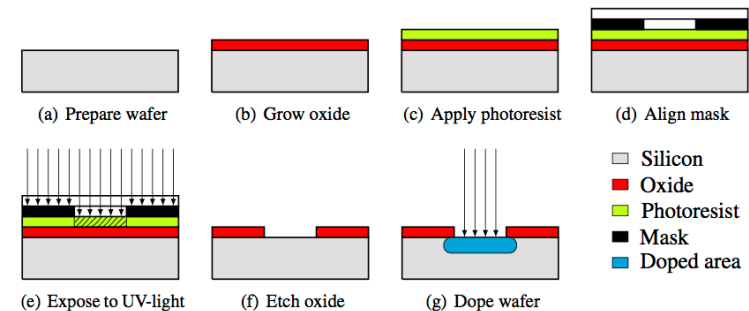Design rule check (DRC)  
Layout verse schematic(LVS)



(Source: MTK)



# Cell-based Design Flow Summary

## RTL Design

Plan the furniture you want to own in your room

## Synthesis





Choose the suitable furniture based on datasheet

## P&R

Procedure Floorplan and Layout of your room

## Fabrication

Construction and get your new room

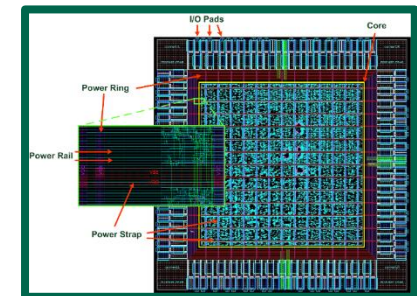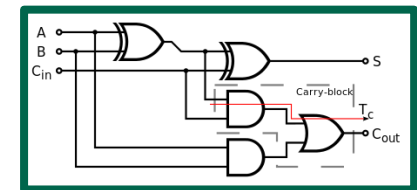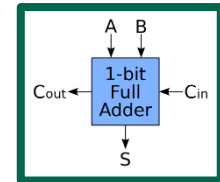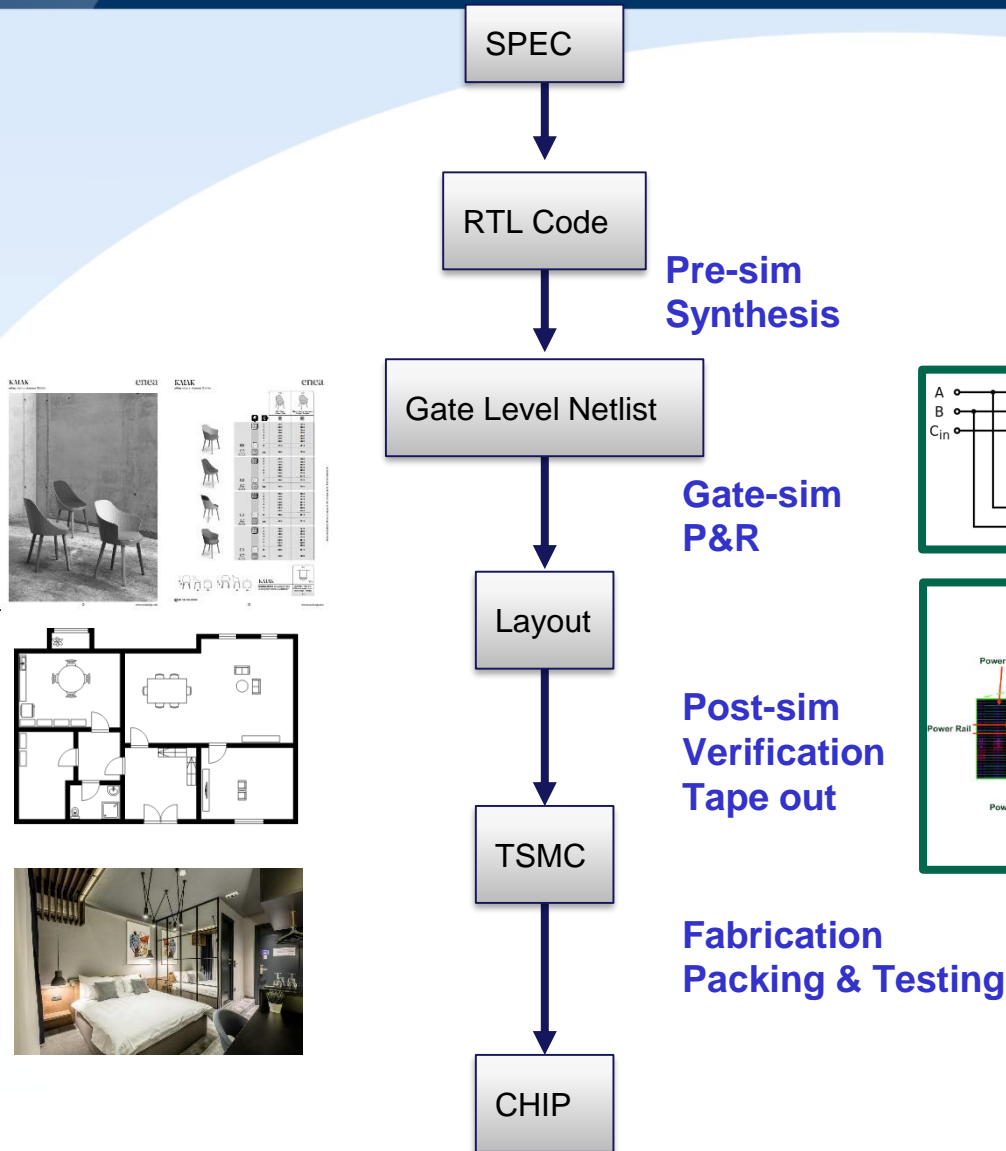

# Cell-based Design Tools

## ✓ System and behavioral description (math. or building module )

- C/C++ / python
- Matlab
- ...

## ✓ Hardware based description language

- System C
- SystemVerilog
- Verilog
- ...

## ✓ RTL simulation and debug

- NC-Verilog, irun
- nLint, Verdi
- ...

## ✓ Synthesis and Verification

- Synopsys
  - RTL Compiler, Design Compiler
  - PrimeTime, SI and StarRC™.
- Cadence
  - BuildGates Extreme
  - Verplex (Formal Verification)
- ...

## ✓ Physical Design and post-layout simulation


- Innovus (SoC Encounter)
- IC compiler
- Calibre
- Nanosim, HSIM, UltraSim: a high-performance transistor-level FastSPICE circuit simulator ...

# Outline

- ✓ Section 1 Introduction to design flow
- ✓ **Section 2 Basic Description of Verilog**
- ✓ Section 3 Behavior Models of Combinational circuit
- ✓ Section 4 Simulations



# Performance Power Area

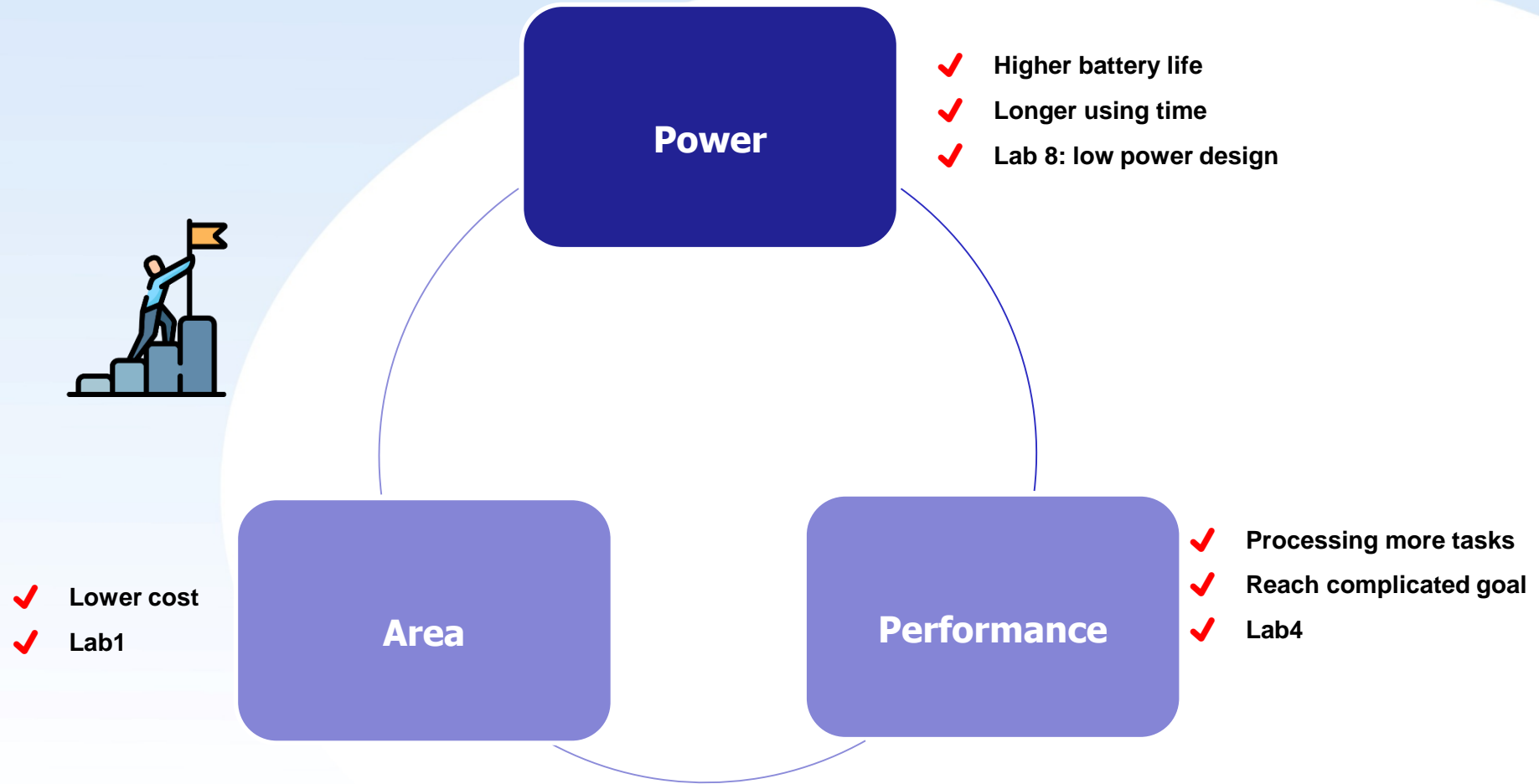

# What is Verilog?

✓ **Hardware** Description Language

✓ **Hardware** Description Language

✓ **Hardware** Description Language



# Hardware vs. Software

## Hardware Parallel

```
module a();  
  b b1();  
  c c1();  
  ...  
endmodule  
  
module b();  
  ...  
endmodule  
  
module c();  
  ...  
endmodule
```

## Software Sequential

```
void a(){...}  
void b(){  
  a();  
  ...  
}  
void c(){  
  a();  
  b();  
}
```

# Hardware Description Language

## ✓ Hardware Description Language

- HDL is a kind of language that can “describe” the hardware module we plan to design
- Verilog and VHDL are both widely using in the IC company
- **The difference between HDL and other programming language is that we must put the “hardware circuit” in our brain during designing the modules**



# Verilog


- ✓ **Basic Language Rules**
- ✓ **Data type**
- ✓ **Port Declare and Connect**
- ✓ **Number Representation**
- ✓ **Operators**
- ✓ **Conditional Description**
- ✓ **Concatenation**





# Module


✓ All modules run **concurrently**

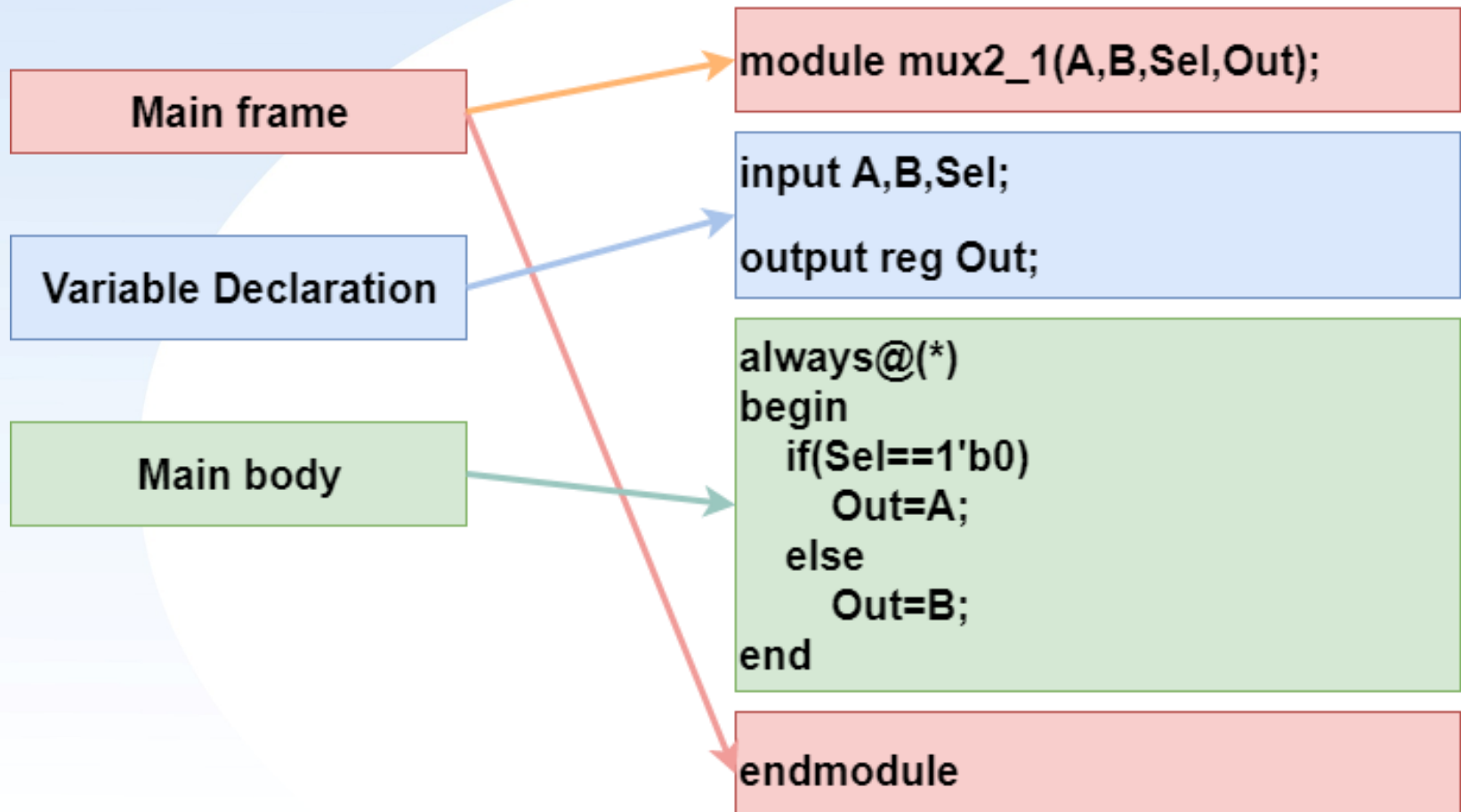

# Combinational Circuits

- ✓ The output of combinational circuit depends on the **present input** only.
- ✓ Combinational circuit can be used to do mathematical computation and circuit control.

Combinational circuit

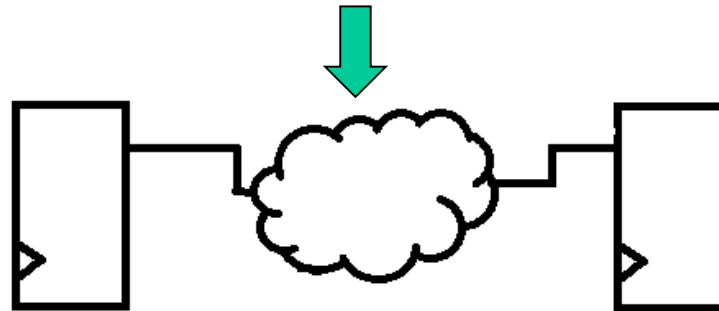


# Procedural block

✓ always, initial
 
## DESIGN.v

```
always@* begin
  if(Q==2'd1)
    A=B;
  else if(Q==2'd2)
    A=C;
  else
    A=D;
end
```




## PATTERN.v

```
module PATTERN(sel,out,a,b);

input out;
output a,b,sel;

reg a,b,sel,clk,reset;

 initial begin
  a=0;
  b=0;
  sel=0;
  reset=0;
  clk=0;
end
```




# Behavioral Modeling (1/3)

## ✓ Data Assignment

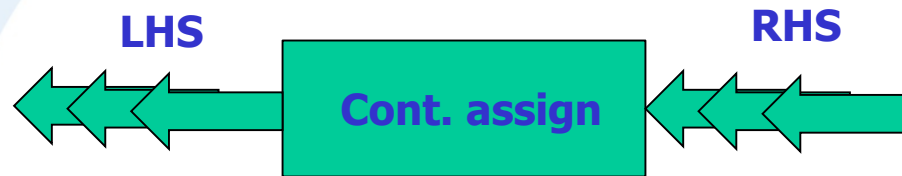
## ✓ Continuous Assignment → for wire assignment

- Imply that whenever any change on the RHS of the assignment occurs, it is evaluated and assigned to the LHS. → **assign**


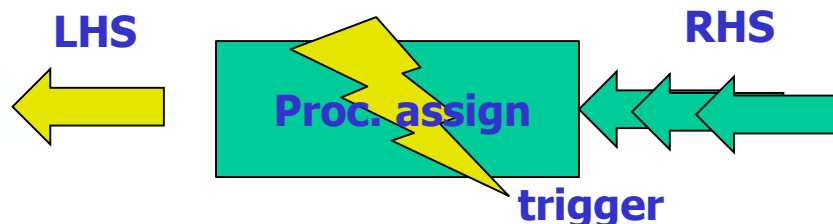
## ✓ Procedural Assignment → for reg assignment

- assignment to "**register**" data types may occur within **always**, **initial**, **task** and **function**. These expressions are controlled by triggers which cause the assignment to evaluate.



# Behavioral Modeling (2/3)

## ✓ Using **always** construct (Proc. assignment)

- assignment should be applied in **topological** order
- Simulation from top to down


– always@(a,b,x,c,d) begin

– x = a & b;

– y = x | c | d;

– end

trigger

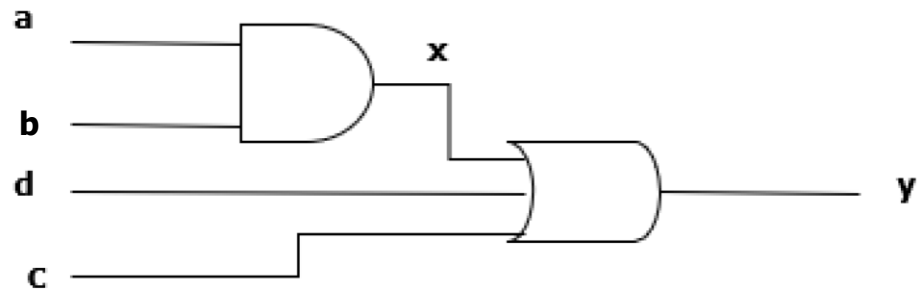

## ✓ Using **assign** construct (Cont. assignments)

- assign y = x | c | d ;
- assign x = a & b ;

Which is better? ?

# Behavioral Modeling: Example (3/3)

- ✓ Using blocking assignments in always construct
  - ✓ The "always" block runs once whenever a signal in the
  - ✓ Sensitivity list changes value (trigger)

```
always@(a or b or c) begin
    x = a & b;
    y = x | c | d;
end
// simulation-synthesis mismatch

always@(a or b or c or d) begin
    y = x | c | d;
    x = a & b;
end // not in topological
// simulation-synthesis mismatch


always@(a or b or c or d or e)
begin
    x = a & b;
    y = x | c | d;
end
//performance loss
```

```
always@(a or b or c or d)
begin
    x = a & b;
    y = x | c | d;
end
// best final

always@(a or b or c or d or x)
begin
    x = a & b;
    y = x | c | d;
end
// correct

always@*
begin
    x = a & b;
    y = x | c | d;
end
// use this!!
```

Better

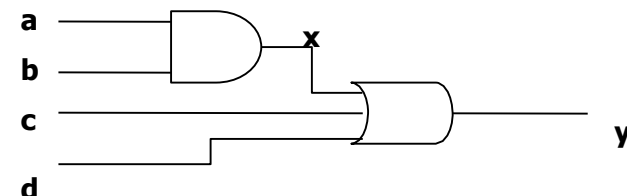

# Basic Language Rules

✓ Terminate lines with **semicolon ;**

## ✓ Identifiers

- Verilog is a **case sensitive** language
  - **C\_out\_bar** and **C\_OUT\_BAR**: two different identifiers
- Starts only with a letter or an **\_**(underline), can be any sequence of letters, digits, \$, **\_**.
  - e.g. 12\_reg ➔ **illegal !!!!**

## ✓ Comments

- single line : **//**
- multiple line : **/\* ... \*/**

```
//assign o_valid = o_valid_r;  
assign o_data = o_data_r;  
assign o_overflow = o_overflow_r;
```

```
/*  
assign o_valid = o_valid_r;  
assign o_data = o_data_r;  
assign o_overflow = o_overflow_r;  
*/
```



# Naming Conventions

## ✓ Common

- Lowercase letters for **signal** names
- Uppercase letters for **constants**

```
parameter IDLE      = 'd0;  
parameter INPUT     = 'd1;  
parameter SET_OP    = 'd2;
```

## ✓ Abbreviation

- **clk** sub-string for clocks
- **rst** sub-string for resets

```
input      clk;  
input      rst_n;
```

## ✓ Suffix

- **\_n** for active-low, **\_z** for tri-state, **\_a** for async , ...
- Ex: `rst_n =>` reset circuit at active-low

## ✓ State Machine

- **[name]\_cs** for current state, **[name]\_ns** for next state

## ✓ Identical(similar) names for connected signals and ports







# Data Type (1/5)
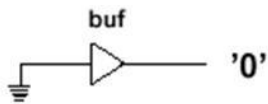
## ✓ 4-value logic system in Verilog: 0, 1, X, or Z


- **0,1:** means low or high signal
- **X:** unknown signal, means that we don't know whether the signal is 0 or 1
- **Z:** high-impedance, the signal is neither 0 nor 1.
- **Avoid X and Z !!!**



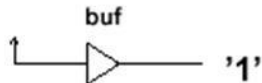
'0', Low, False, Logic Low, Ground, VSS,  
Negative Assertion



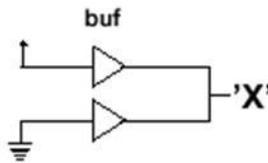
'1', High, True, Logic High, Power,  
VDD, VCC, Positive Assertion



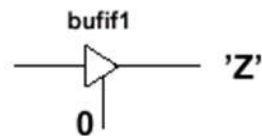'X' Unknown: Occurs at Logical Which Cannot  
be Resolved Conflict



HiZ, High Impedance, Tri- Stated,

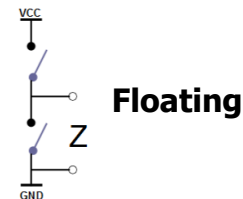

# Data Type (2/5)

## ✓ **Wire** (default = **Z** (high impedance, floating net))

A wire cannot store value, often use in combination circuit

### 1. Represent port connection between devices

```
wire clk,A,B;  
BBQ bbq1(.clk(clk),.meat(A),.vegetable(B))  
BBQ bbq2(.clk(clk),.meat(A),.vegetable(B))
```

### 2. Can not be use in procedure assignment: 'initial' or 'always'

```
wire C;  
always@(*) begin  
    C = a+b; // wrong, C should be reg data type (X)  
end
```

### 3. Only use in continuous assignment: 'assign'

```
wire C;  
assign C = a+b; // correct (O)
```



# Data Type (3/5)

## ✓ Registers (default = **X** (unknown, should be initialized) )

A reg is a simple Verilog, variable-type register  
represent abstract data storage element

Hold their value until explicitly assigned in an initial or always block

1. Only use in procedure assignment: 'initial' or 'always'
2. Does not imply a physical register

- EX1

```
reg C;  
always@(*) begin  
    C = a+b;  
end
```

// (0) **This reg does not imply a physical register**

- EX2

```
reg C;  
Always@(posedge clk) begin  
    C <= a+b;  
end
```

// (0) **This reg imply a physical register**



# Data Type (4/5)

## Wire

1. Port connection(in/out)
2. Assign (cont. assignment)
3. Can declared as vector
4. Often use in Comb. circuit

## Reg


1. Port output(register out)
2. Always block (Proc. assignment)
3. Can declared as vector
4. Often use in Sequ. circuit



# Data Type (5/5)
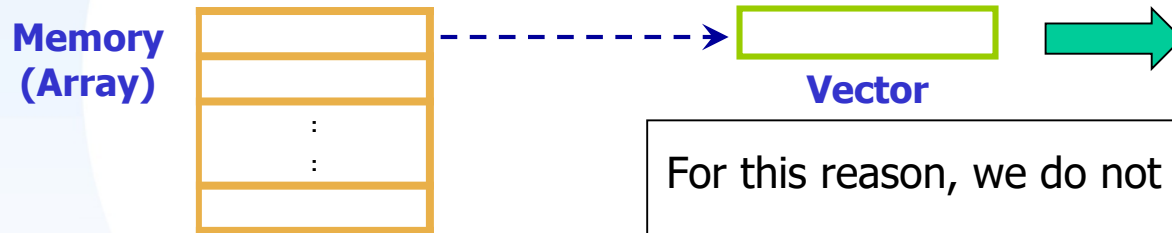
## ✓ Vectors and Arrays : the **wire** and **reg** can be represented as a vector

- Vectors: single-element with multiple-bit
  - `wire [7:0] vec;` → 8-bit
- Arrays: multiple-element with multiple-bit
  - It isn't well for the backend verifications
  - `reg [7:0] mem [1023:0]` → Memories (1k - 1byte)



For this reason, we do not use array as memory,  
Memory component will be introduced later

# Port Declare and Connect (1/3)


## ✓ Interface is defined by ports

### – Port inside module declaration

- ◆ **input** : input port, **only wire** can be assigned
- ◆ **output** : output port, **wire/reg** can be assigned
- ◆ **inout** : bidirectional port, **only wire** can be assigned
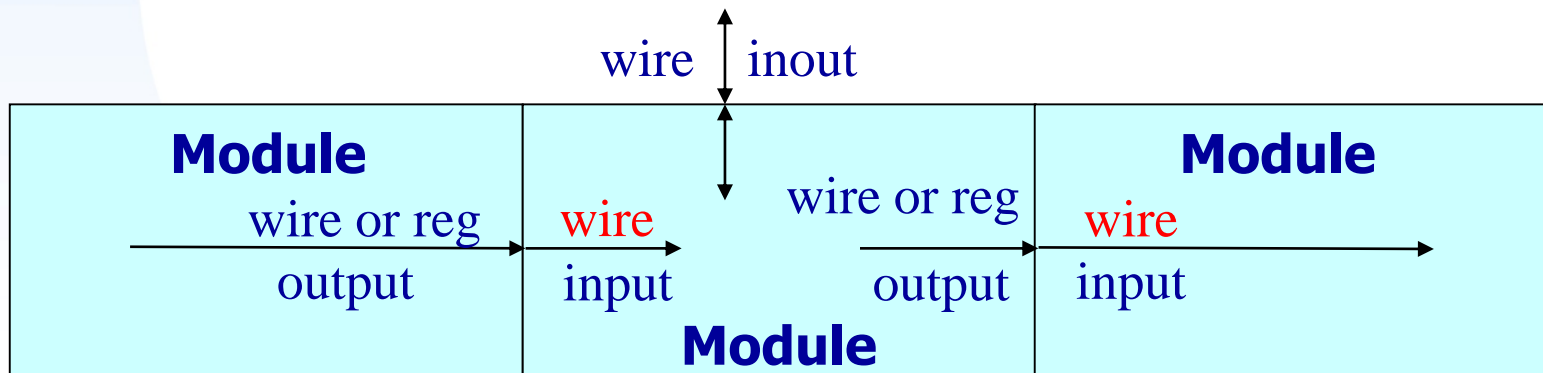
### – Port connection outside module

- ◆ **input** : wire or reg can be assigned to connect into the module
- ◆ **output** : only wire can be assigned to connect out of the module
- ◆ **inout** : register assignment is forbidden neither in module nor out of module [Tri-state]




# Port Declare and Connect (2/3)

## ✓ Modules connected by port order (implicit)

- Order must match correctly. Normally, it not a good idea to connect ports implicitly. It could **cause problem** in debugging when any new port is added or deleted.
- e.g. : `FA U01( A, B, CIN, SUM, COUT );`

**Order is vital!**

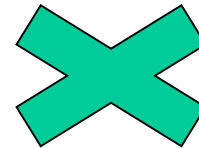


## ✓ Modules connect by name (explicit)

- Use **named mapping** instead of positional mapping
- name shall match correctly.
- e.g. : `FA U01 ( .a(A), .b(B), .cin(CIN), .sum(SUM), .cout(COUT) );`

Use this!!!

**Name Mapping**

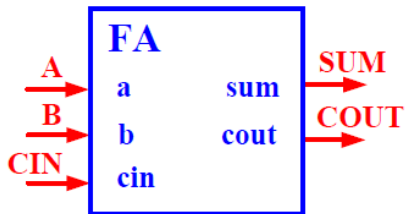

# Port Declare and Connect : Example (3/3)

```
module MUX2_1(out,a,b,sel,clk,rst);  
input      sel,clk,rst;  
input reg a,b;  
output reg out;  
wire      c;  
//incorrect define  
  
//Continuous assignment  
assign c = (sel==1'b0)?a:b;  
  
//Procedural assignment,  
//only reg data type can be assigned value  
always@(posedge rst or posedge clk)  
begin  
    if(reset==1'b1) out <= 0;  
    else out <= c;  
end  
endmodule
```

Wire for input

【 sub module 】

```
`include "mux.v"  
module test;  
reg      out; //incorrect define  
reg      a,b;  
reg      clk,sel,rst;
```

Wire for connection


// 1. connect port by ordering  
MUX2\_1 **mux**(out,a,b,sel,clk,rst);

// 2. connect port by name  
MUX2\_1 **mux**(.clk(clk), .reset(rst),  
.sel(sel), .a(a), .b(b), .out(**out**));

initial begin Name submodules differently

```
.....  
end  
endmodule
```

【 test module 】

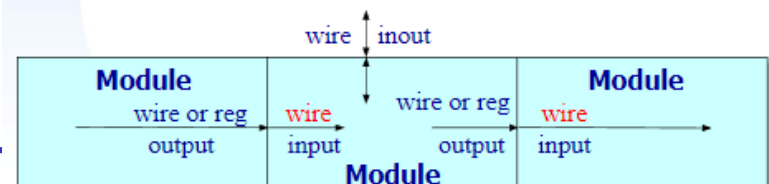



# Number Representation (1/2)

## ✓ Number Representation

### – Format: `<size>'<base><value>`

- Base format: b(binary), o(octal), d(decimal) or h(hexadecimal)
  - ◆ e.g. `4'd10 = 4'1010 = 4'o12 = 4'ha` → 10, decimal
- If `<size>` is smaller than `<value>`, left-most bits of `<value>` are truncated
  - ◆ e.g. `6'hca` → 6-bit, store as `6'b001010` (truncated, not `11001010`!)
- If `<size>` is larger than `<value>`, then left-most bits are filled based on the value of the left-most bit in `<value>`
  - ◆ Left most '0' or '1' are filled with '0', 'Z' are filled with 'Z' and 'X' with 'X'
  - ◆ e.g. `12'hz` → `zzzz zzzz zzzz`; `6'bx` → `xx xxxx`;  
`8'b0` → `0000 0000`; `8'b1` → `0000 0001`;
  - ◆ e.g. `6'ha` → 6-bit, store as `6'b001010` (filled with 2-bit '0' on left!)
- Default size is 32-bits decimal number
  - ◆ e.g. `11` → `32'd11` (integer type)



# Number Representation(2/2)

## ✓ Number Representation

### – Signed Value (Verilog-2001)

- By default the signal is unsigned → Declare with keyword “signed”
  - ◆ e.g. wire **signed** [7:0] a;
- Negative : -<size>'<base><value>
  - ◆ e.g. -8'd3 → legal, 8'd-3 → illegal
  - ◆ A 3-bit signed value would be declared as wire signed [2:0] A

Decimal Value	Signed Representation (2's complement)
3	3'b011
2	3'b010
1	3'b001
0	3'b000
-1	3'b111
-2	3'b110
-3	3'b101
-4	3'b100



# Operators (1/4)

## ✓ Operators

### – Arithmetic Description

- $A = B + C;$
- $A = B - C;$
- $A = B * C;$
- $A = B / C;$
- $A = B \% C;$  (modulus)

### – Shift Operator (**logical**)

- $A = B >> 2;$  ➔ shift right 'B' by 2-bit (if  $B = 4'b1000$ ,  $A = 4'b0010$ )
- $A = B << 2;$  ➔ shift left 'B' by 2-bit (if  $B = 4'b0001$ ,  $A = 4'b0100$ )

### – Shift Operator (**arithmetic**)

- $A = B >>> 2;$
- $A = B <<< 2;$
- e.g. wire signed [3:0] A,B;

">>>", "<<<" are used only for 'signed' data type in Verilog 2001

$B = 4'b1000;$

$A = B >>> 2;$

( $A = 4'b1110$ , which is 1000 shifted to the right two positions and sign-filled.)



# Operators (2/4)

## ✓ Unsigned Operation

```
wire [7:0] a,b;  
wire [3:0] c,  
wire [8:0] sum1, sum2, sum3, sum4;
```

```
assign sum1 = a + b;  
assign sum2 = a + c;  
assign sum3 = a + {4{1'b0}}, c};
```

a and b are same width =>  
can be applied to signed and unsigned

reg type is regard as unsigned =>  
automatic 0 extension

manual 0 extension

## ✓ Signed Operation

```
wire signed [7:0] a,b;  
wire signed [3:0] c_sign;  
wire signed [8:0] sum1, sum4;
```

```
assign sum1 = a + b;  
assign sum4 = a + c_sign;
```

a and b are same width =>  
can be applied to signed and unsigned

c\_sign is signed type =>  
automatic signed extension

```
wire [7:0] a,b;  
wire [3:0] c,  
wire [7:0] sum1, sum4;
```

```
assign sum4 = a + {4{c[3]}}, c};
```


manual signed extension

the same !!

# Operators (3/4)
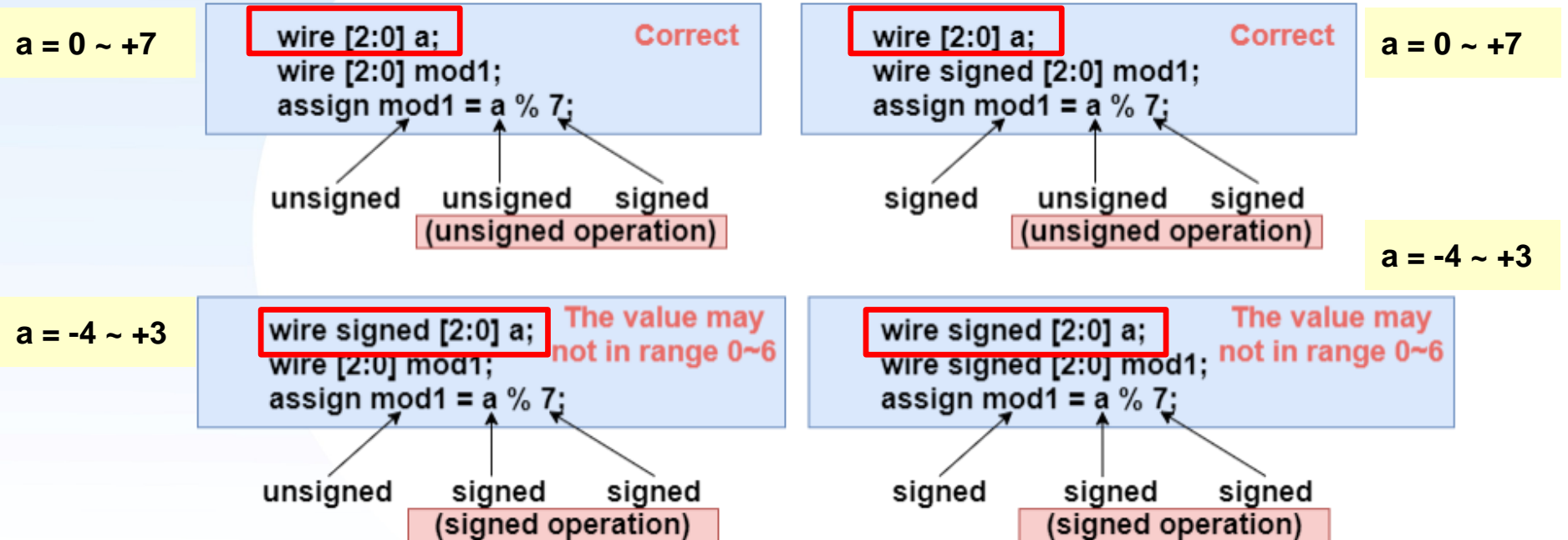
## ✓ Unsigned / Signed Mix Operation

- If there are one unsigned operator, the operation will be regard as **unsigned**
- Example:
  - Goal: Number need to be in 0~6



# Operators (4/4)

- ✓ **Bitwise operators:** perform bit-sliced operations on vectors
  - $\sim(4'b0101) = \{\sim 0, \sim 1, \sim 0, \sim 1\} = 4'b1010$
  - $4'b0101 \& 4'b0011 = 4'b0001$
- ✓ **Logical operators:** return one-bit (true/false) results
  - $!(4'b0101) = \sim 1 = 1'b0$
- ✓ **Reduction operators:** act on each bit of a single input vector
  - $\&(4'b0101) = 0 \& 1 \& 0 \& 1 = 1'b0$
- ✓ **Comparison operators:** perform a Boolean test on two arguments

Bitwise	Logical	Reduction	Comparison																																
<table><tr><td>~a</td><td>NOT</td></tr><tr><td>a &amp; b</td><td>AND</td></tr><tr><td>a   b</td><td>OR</td></tr><tr><td>a ^ b</td><td>XOR</td></tr><tr><td>a ~^ b</td><td>XNOR</td></tr></table>	~a	NOT	a & b	AND	a   b	OR	a ^ b	XOR	a ~^ b	XNOR	<table><tr><td>!a</td><td>NOT</td></tr><tr><td>a &amp;&amp; b</td><td>AND</td></tr><tr><td>a    b</td><td>OR</td></tr></table>	!a	NOT	a && b	AND	a    b	OR	<table><tr><td>&amp;a</td><td>AND</td></tr><tr><td>~&amp;</td><td>NAND</td></tr><tr><td> </td><td>OR</td></tr><tr><td>~ </td><td>NOR</td></tr><tr><td>^</td><td>XOR</td></tr></table>	&a	AND	~&	NAND		OR	~	NOR	^	XOR	<table><tr><td>a &lt; b a &gt; b a &lt;= b a &gt;= b</td><td>Relational</td></tr><tr><td>a == b a != b</td><td>[in]equality returns x when x or z in bits. Else returns 0 or 1</td></tr><tr><td>a === b a !== b</td><td>case [in]equality returns 0 or 1 based on bit by bit comparison</td></tr></table>	a < b a > b a <= b a >= b	Relational	a == b a != b	[in]equality returns x when x or z in bits. Else returns 0 or 1	a === b a !== b	case [in]equality returns 0 or 1 based on bit by bit comparison
~a	NOT																																		
a & b	AND																																		
a   b	OR																																		
a ^ b	XOR																																		
a ~^ b	XNOR																																		
!a	NOT																																		
a && b	AND																																		
a    b	OR																																		
&a	AND																																		
~&	NAND																																		
	OR																																		
~	NOR																																		
^	XOR																																		
a < b a > b a <= b a >= b	Relational																																		
a == b a != b	[in]equality returns x when x or z in bits. Else returns 0 or 1																																		
a === b a !== b	case [in]equality returns 0 or 1 based on bit by bit comparison																																		

*Note distinction between ~a and !a*

*Note distinction between  $\sim a$  and  $!a$*



# Conditional Description (1/2)

## ✓ **If-then-else** often infers a cascaded encoder

- inputs signals with different arrival time
- Priority inferred
- used in proc. assignment

## ✓ **case** infers a single-level mux

- case is better if priority encoding is not required
- case is generally simulated **faster** than if-then-else
- used in proc. assignment

## ✓ **conditional assignment (? :)**

- `? : ➔ c = sel ? a : b;`
- used in cont. assignment
- same as if-else statement





# Conditional Description: Example (2/2)

## Conditional Assignment (?:)



```
assign data=(Sel==2'b00) ? a:  
((Sel==2'b01) ? b:  
((Sel==2'b10) ? c:  
((Sel==2'b11) ? d)));
```

## If-then-else

```
always@ (*)  
begin  
    if(Sel == 2'b00)  
        data=a;  
    else if(Sel== 2'b01)  
        data=b;  
    else if(Sel==2'b10)  
        data=c;  
    else  
        data=d;  
end
```
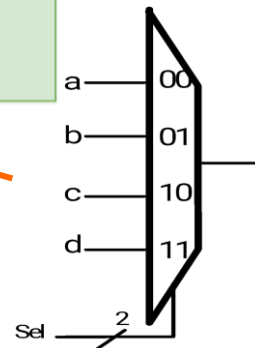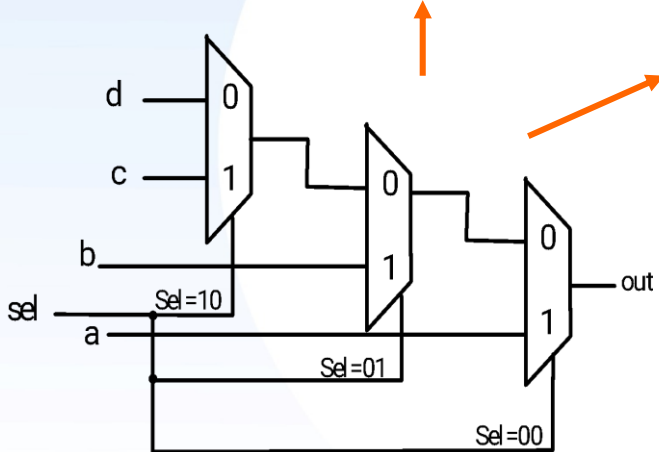
## case


```
always@(*)  
begin  
    case(Sel)  
        2'b00: data = a;  
        2'b01: data = b;  
        2'b10: data = c;  
        default: data = d;  
    endcase  
end
```




# Concatenation
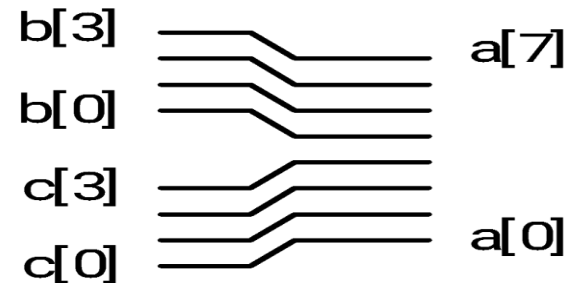
## Concatenation

- $\{ \}$   $\rightarrow$  assign  $a = \{b, c\};$



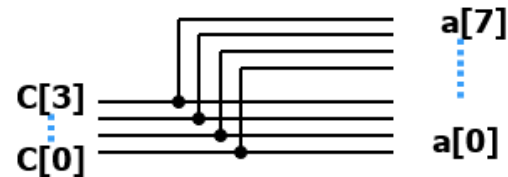- $\{\{\}\}$   $\rightarrow$  assign  $a = \{2\{c\}\};$




- Ex.  $a[4:0] = \{b[3:0], 1'b0\}; \Leftrightarrow a = b \ll 1;$

# Gate-Level Modeling (1/3)

## ✓ Primitive logic gate

- and

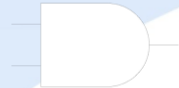


- or



- xor



- nand

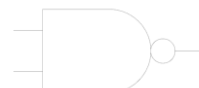

- nor




- xnor




## Bitwise Operator

$\sim a$	NOT
$a \& b$	AND
$a   b$	OR
$a \wedge b$	XOR
$a \sim \wedge b$	XNOR

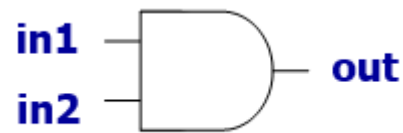can use without instance name → i.e. `and( out, in1, in2 ) ;`



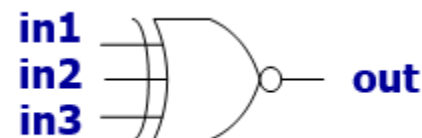can use with multiple inputs → i.e. `xor( out, in1, in2, in3 ) ;`



# Gate-Level Modeling (2/3)

## ✓ Primitive logic gate

- buf,



- bufif0,




- bufif1



- not,




- notif0,

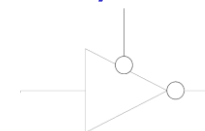


- notif1



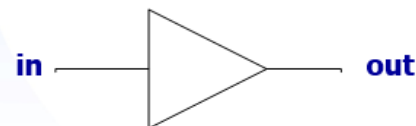can use without instance name → i.e. buf( out, in ) ;



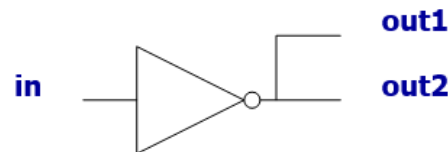can use with multiple outputs → i.e. not( out1, out2 ,in) ;



# Behavioral Model v.s. Gate Level Model


## ✓ Gate Level Model

```
module mux2_1(A,B,Sel,Out);
```

```
input A,B,Sel;  
output Out;  
wire Sel_n, and_out1, and_out2;
```

```
not (Sel_n, Sel);  
and (and_out1, A, Sel_n);  
and (and_out2, B, Sel);  
or (Out, and_out1, and_out2);
```

```
endmodule
```

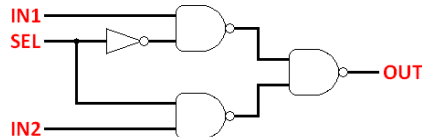


## ✓ Behavioral Model

```
module mux2_1(A,B,Sel,Out);
```

```
input A,B,Sel;  
output reg Out;
```

```
always@(*)  
begin  
    if(Sel==1'b0)  
        Out=A;  
    else  
        Out=B;  
    end  
end
```

```
endmodule
```

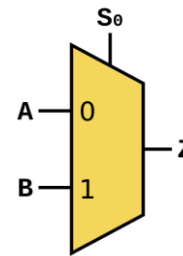

# Coding style

- ✓ Data has to be described in one always block
  - Multi-driver (not synthesizable)

```
always@* begin
```


```
    A=B+C;
```

```
end
```

```
always@* begin
```

```
    A=B+D;
```

```
end
```

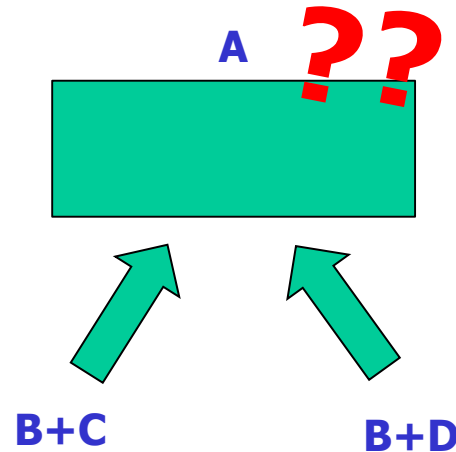

# Coding style

✓ Don't use initial block in your design for synthesis

**initial begin**

**A=B;**

**B=C;**

**end**



**Initial use for PATTERN only!!**



# Coding style

## ✓ Avoid combinational loop

- May synthesis a Latch in your circuit !! (Latch is non-edge triggered, avoid)

```
always@* begin
  A = ~B;
  B = ~C;
  C = ~A;
end
```



```
always@* begin
  case(Q)
    2'd0: A=B;
    2'd1: A=C;
  endcase
end
```



```
always@* begin
  if(Q==2'd1)
    A=B;
  else if(Q==2'd2)
    A=C;
end
```



```
always@* begin
  case(Q)
    2'd0: A=B;
    2'd1: A=C;
    default: A=D;
  endcase
end
```



```
always@* begin
  if(Q==2'd1)
    A=B;
  else if(Q==2'd2)
    A=C;
  else
    A=D;
end
```


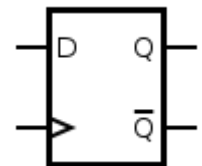
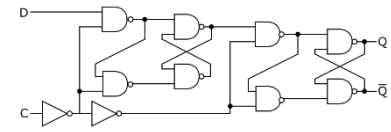
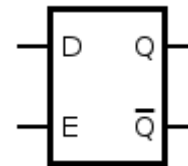
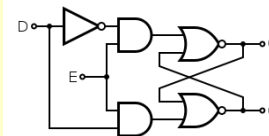



Figure. (a) D-latch (b) D flip-flop
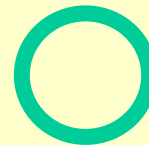
# Outline

- ✓ Section 1 Introduction to design flow
- ✓ Section 2 Basic Description of Verilog
- ✓ Section 3 Behavior Models of Combinational circuit
- ✓ **Section 4 Simulations**



# Simulation Environment

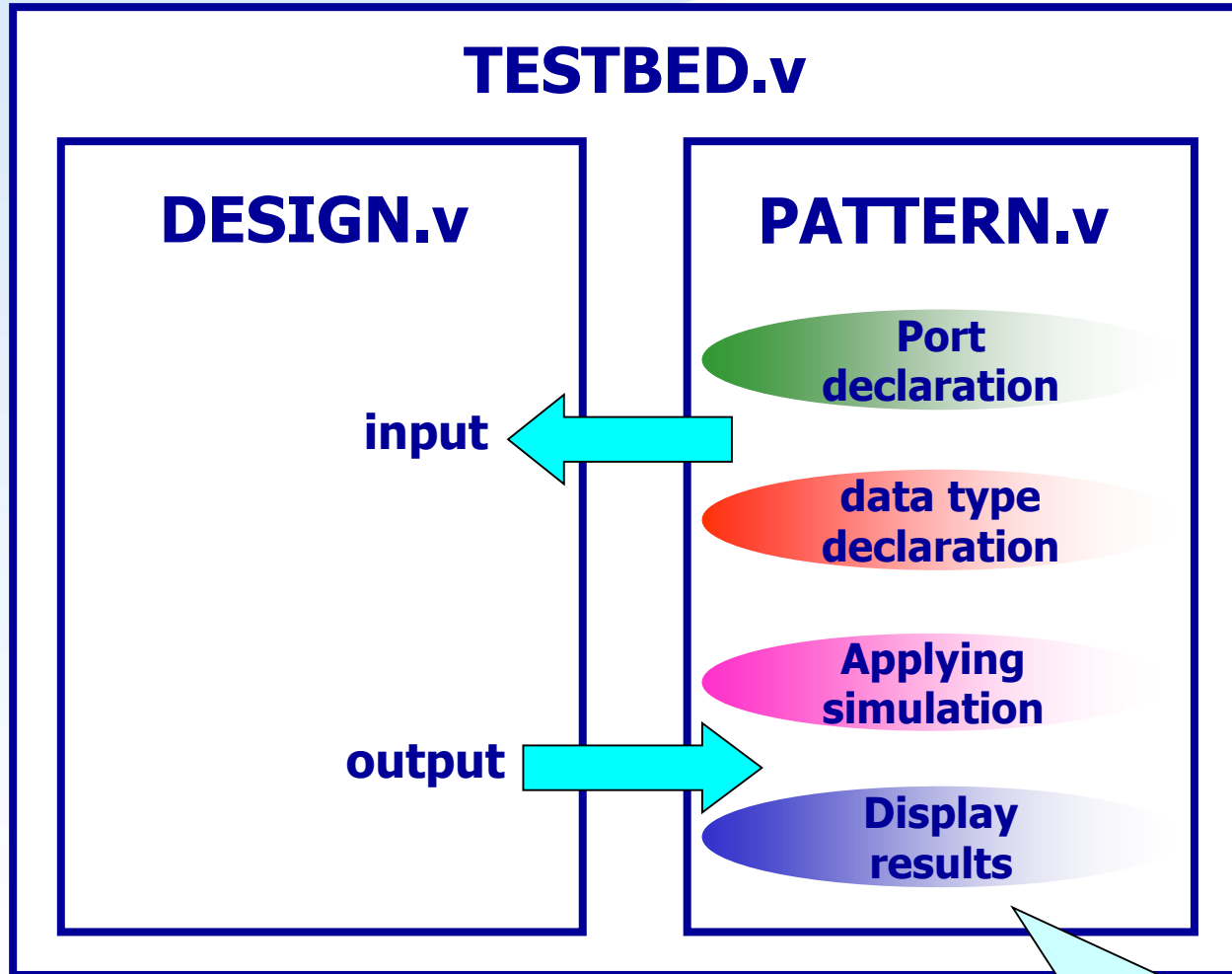

Can use behavior-level



# Simulation Environment (cont.)

## TESTBED.v

```
`timescale 1ns/10ps  
`include "MUX2_1.v"  
`include "PATTERN.v"
```

```
module TESTBED;
```

```
  wire out,a,b,sel,clk,reset;
```

```
  MUX2_1 mux(.out(out),.a(a),.b(b),.sel(sel));  
  PATTERN pat(.sel(sel),.out(out),.a(a),.b(b));
```

```
endmodule
```

← Just like a breadboard

← Putting devices on the board and connect them together!

# Simulation Environment (cont.)

## PATTERN.v

```
module PATTERN(sel,out,a,b);
```

```
input out;  
output a,b,sel;
```

```
reg a,b,sel,clk,reset;
```

```
integer i;  
parameter CYCLE=10;
```

```
always #(CYCLE/2) clk = ~clk;
```

```
initial begin  
a=0;b=0;sel=0;reset=0;clk=0;  
#3 reset = 1;  
#10 reset = 0;
```

```
# CYCLE sel=1;  
for(i=0;i<=3;i=i+1) begin  
#CYCLE {a,b}=i;  
#CYCLE $display( "sel=%b, a=%b, b=%b,  
out=%b" , sel, a, b, out);  
end  
  
# CYCLE sel=0;  
for(i=0;i<=3;i=i+1) begin  
# CYCLE {a,b}=i;  
# CYCLE $display( "sel=%b, a=%b, b=%b,  
out=%b" , sel, a, b, out);  
end  
  
# CYCLE $finish;  
end
```


```
endmodule
```



# Simulation Environment (cont.)

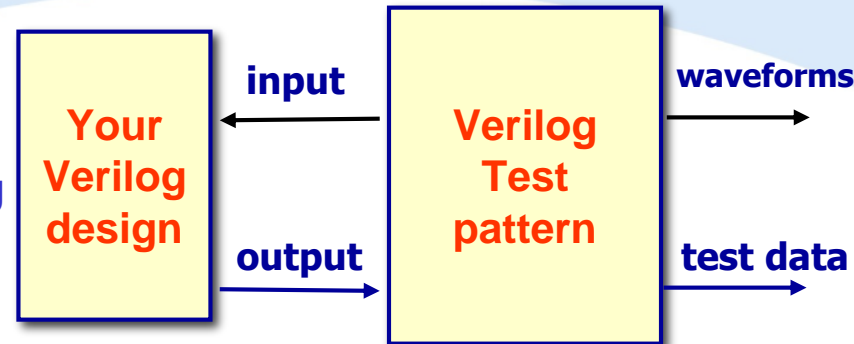
## ✓ Simulation command

- Verilog compile
  - `irun TESTBED.v -define RTL -debug`
- Invoke nWave
  - `nWave &`
- Stop the simulation and continue the simulation
  - `Ctrl+z` ➔ Suspend the simulation at anytime you want. (not terminate yet!)
  - `jobs on` ➔ Here you can see the jobs which are processing with a index the left [JOB\_INDEX]
  - `kill` ➔ Use the command "`kill %JOB_INDEX`" to terminate the job



# nWave

## ✓ Overview

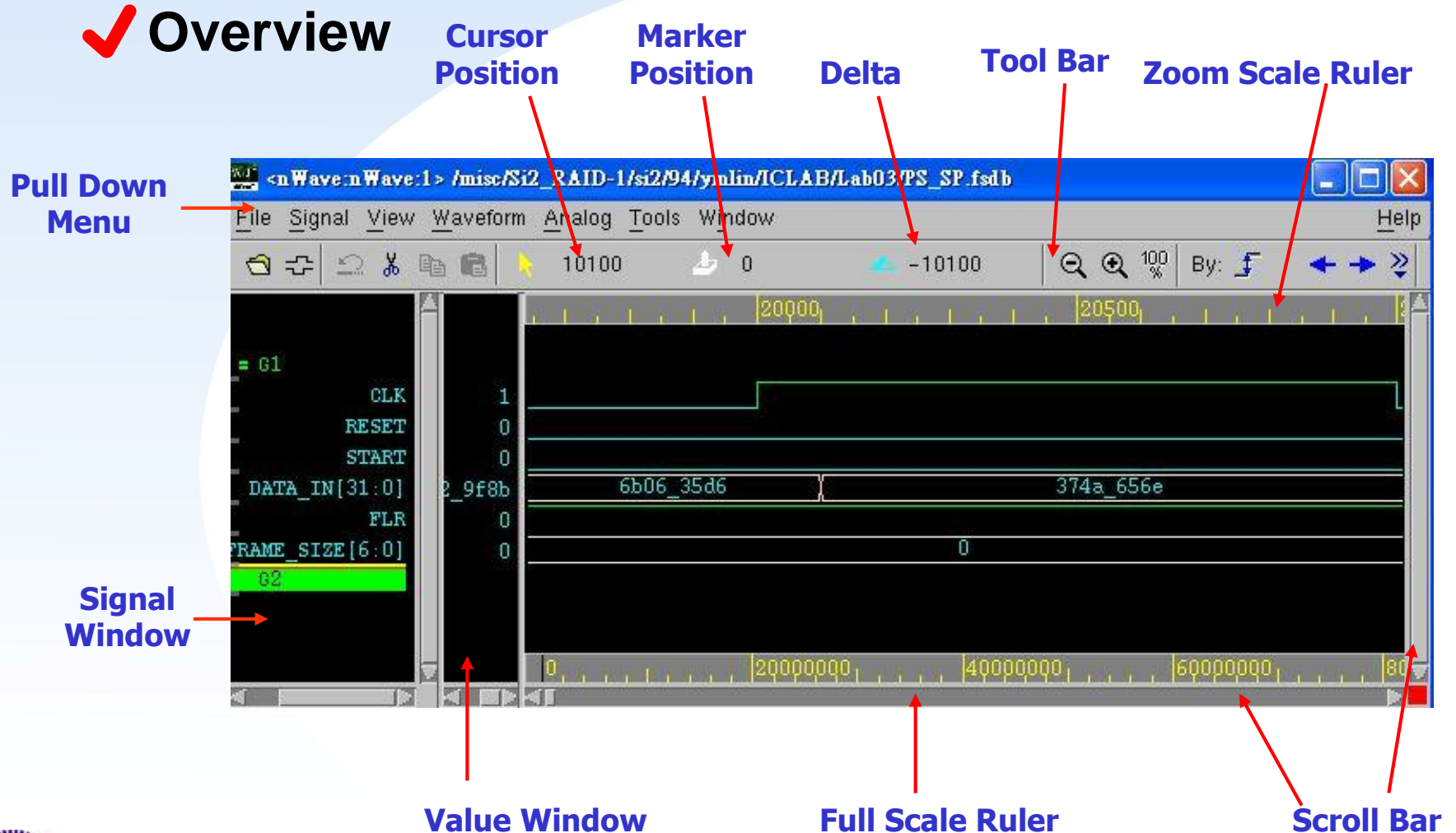




# nWave (cont.)

## ✓ Open fsdb file


- Use **File** → **Open...** command

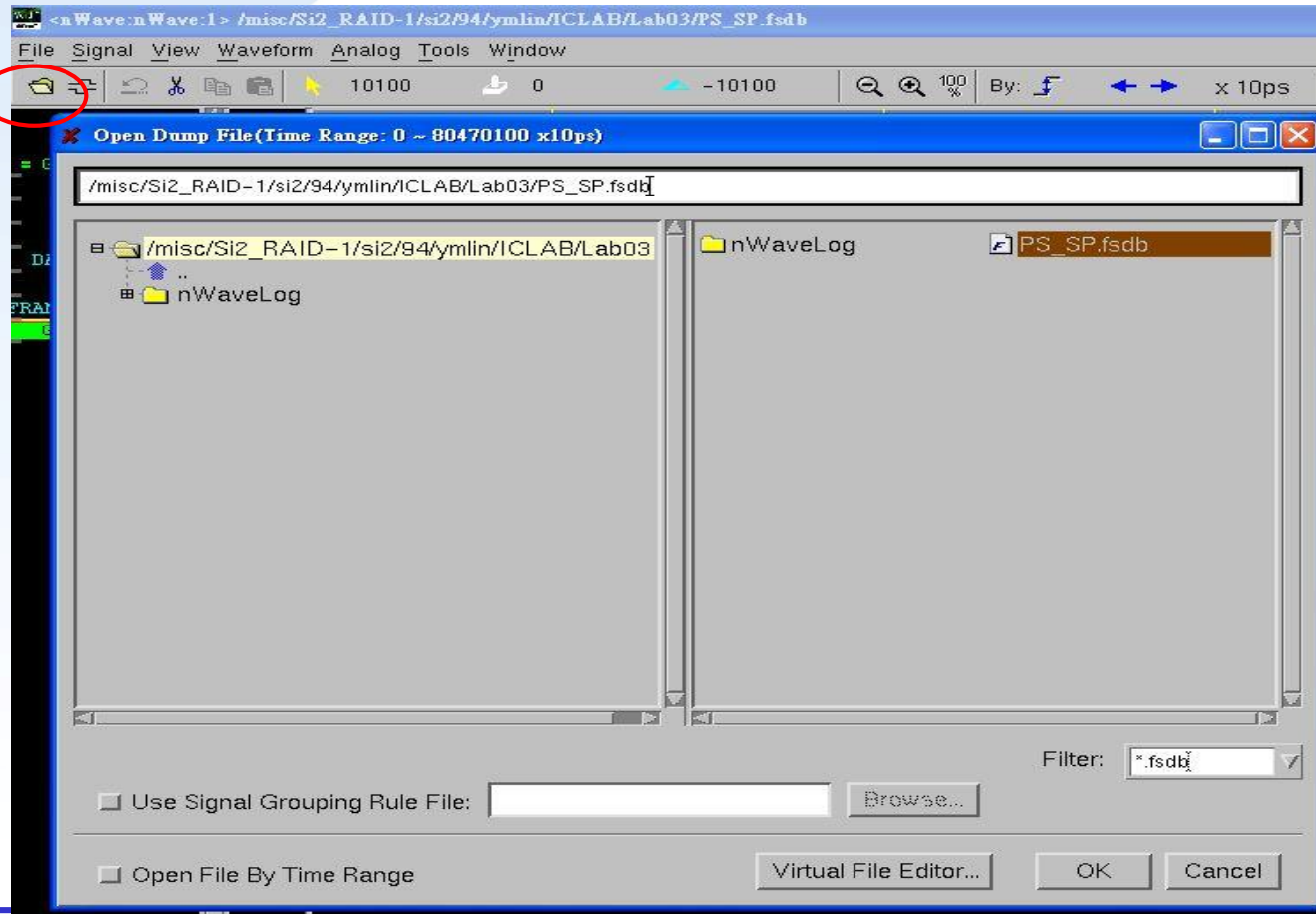

# nWave (cont.)
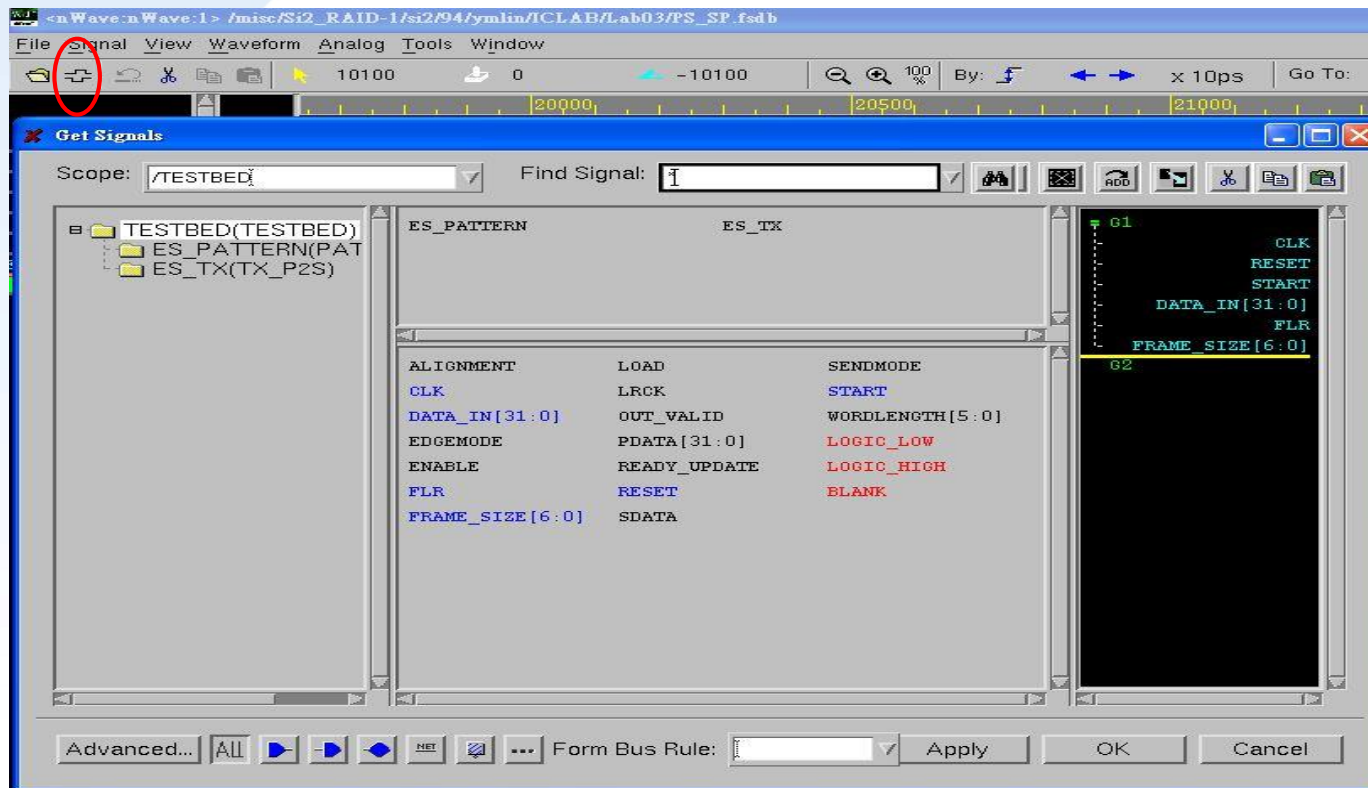
## ✓ Get signal

- Use **Signal** → **Get Signals...** command






## ✓ Choose value format

- On the value window click Left Button



**Default : Hexadecimal**

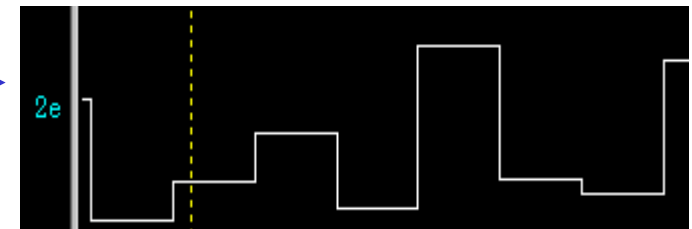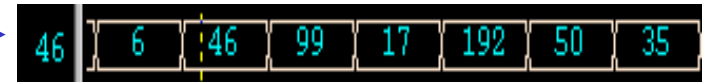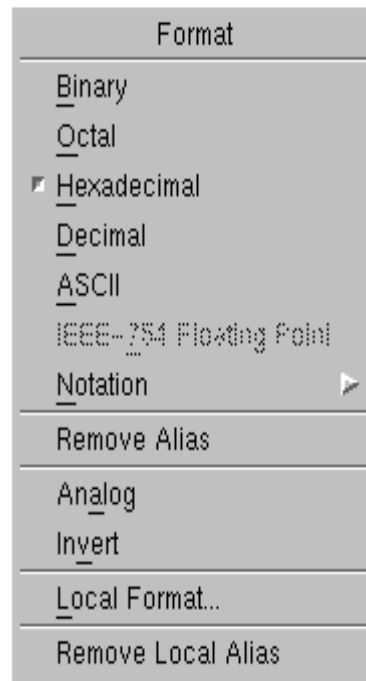

# nWave (cont.)

## ✓ Reload nWave

- Update fsdb file in Debussy database
  - **File** → **Reload**
  - **Hot key** → **L (shift + I)**

